

Powering the internet of things

Yogesh Ramadass

Texas Instruments


Trends in low-power electronics

Increasing Energy Criticality


Portable Computers



Wearable Devices

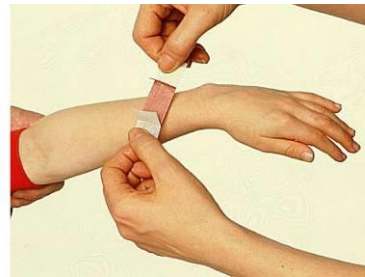

Implantables

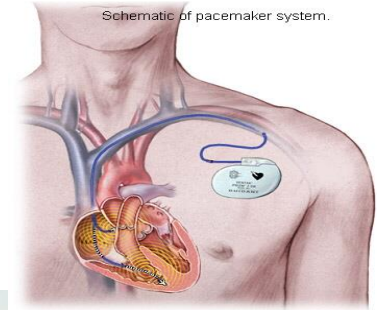

Handhelds




Sensor Networks

- Issues - Size, weight, operating lifetime
- Energy efficiency of IC's is crucial


IoT Node for Monitoring

Component	Power	Comments
Inst. Amplifier [Verma, VLSI09]	3.5 μ W	1V V_{DD} , 1.3 μ V _{rms} input referred noise
ADC [Yaul, ISSCC14]	3.7 μ W	1V V_{DD} , 450kS/s, 9.8ENOB
16b μ -cont [Kwong, ISSCC08]	2.72 μ W	0.5V V_{DD} , 128kb SRAM, 100kHz
Radio [CC 2550]	33.6mW (active)	3V V_{DD} , 2.4GHz, -12dBm P_{OUT}

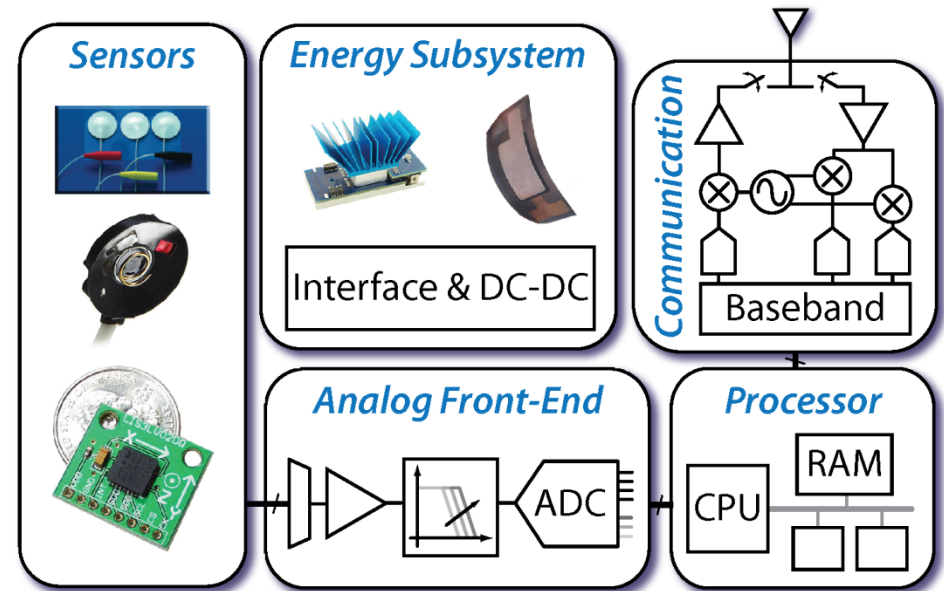


- Power consumption of building blocks steadily decreasing
- Low voltage operation, multi-cores, local processing of information, aggressive duty cycling

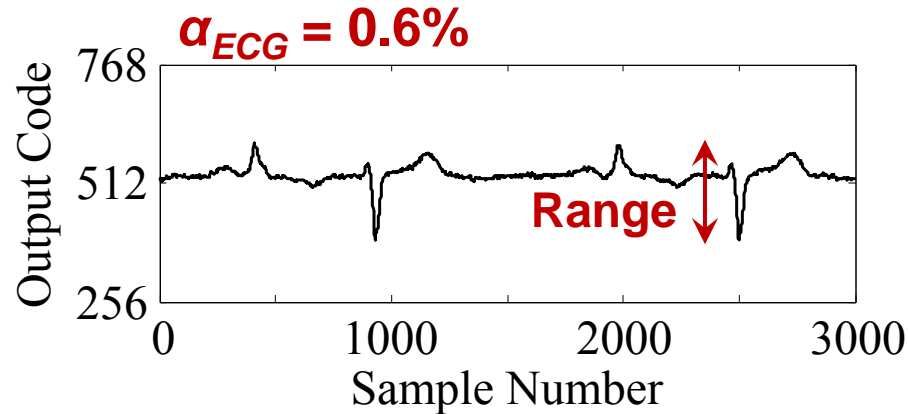LSB-first SAR ADC for Low-Activity Signals



ECG Signal, 1 kS/s

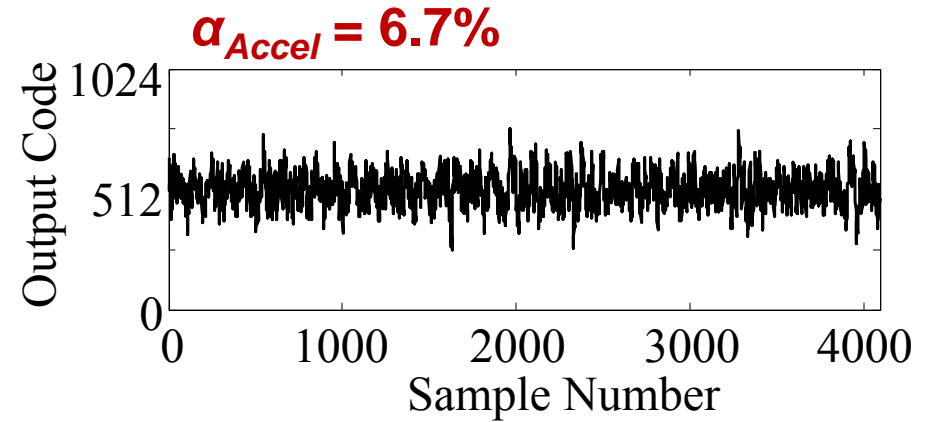

Vibration Signal, 5 kS/s

Range is given for best case (DC) and worst case (fullscale Nyquist sinusoid) inputs.


[F. Yaul, ISSCC 2014]

Technology	0.18 μ m		
Unit Capacitor (fF)	72		
Supply Voltage (V)	1.0	0.6	0.5
Sample Rate (Hz)	450k	16k	4k
ENOB (bit)	9.82	9.73	9.55
Power (W)	3.7–13 μ	47–170n	8.7–31n
FoM (fJ)	9.1–35	3.5–20	2.9–17



LSB-first predictive algorithm for reduced power

Reduced radio consumption

Epileptic Seizure Onset Detection

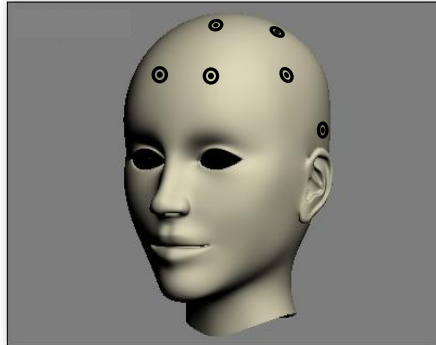

On-scalp Field Potentials (EEG):

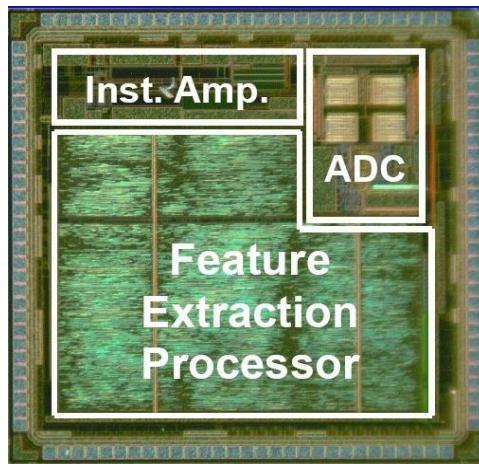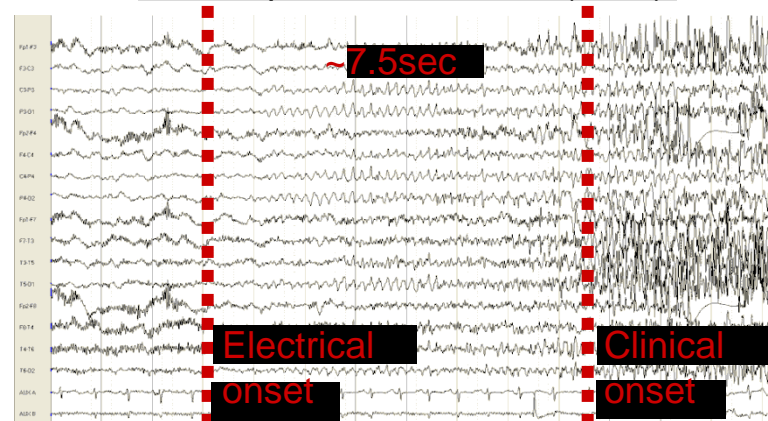

	Conventional-Wireless EEG	Using Local Processing
Capture	75 μ W	75 μ W
Digital processing	--	2 μ W
Radio	1733 μ W	43 μ W
Total	1808 μ W	120 μ W


Computation vs. Communication Trade-off

Self-Powered Applications

Low data rate, low duty cycle, ultra-low power



Solar Keyboard

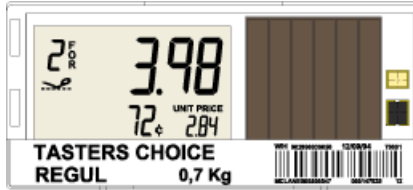


Electronic Shelf Labels



Self-powered switches



Occupancy Sensor

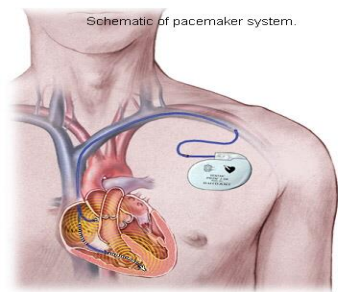

Implantables



Pipelines



Oil Rig

Environmental Awareness




Smoke Detector



Structural sensors

Hard to Reach

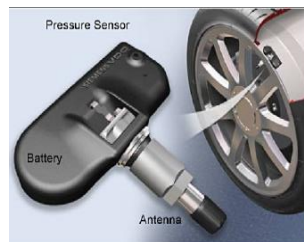


TPMS

Outline

- Energy Sources and Characteristics
 - Energy Harvesting System
 - Solar
 - Thermal
 - Vibration
- Energy Storage Options
- Energy Management Circuits
 - Chargers
 - DC/DC Converters
 - Battery Management
 - Peripherals
- Summary

Battery Operated System

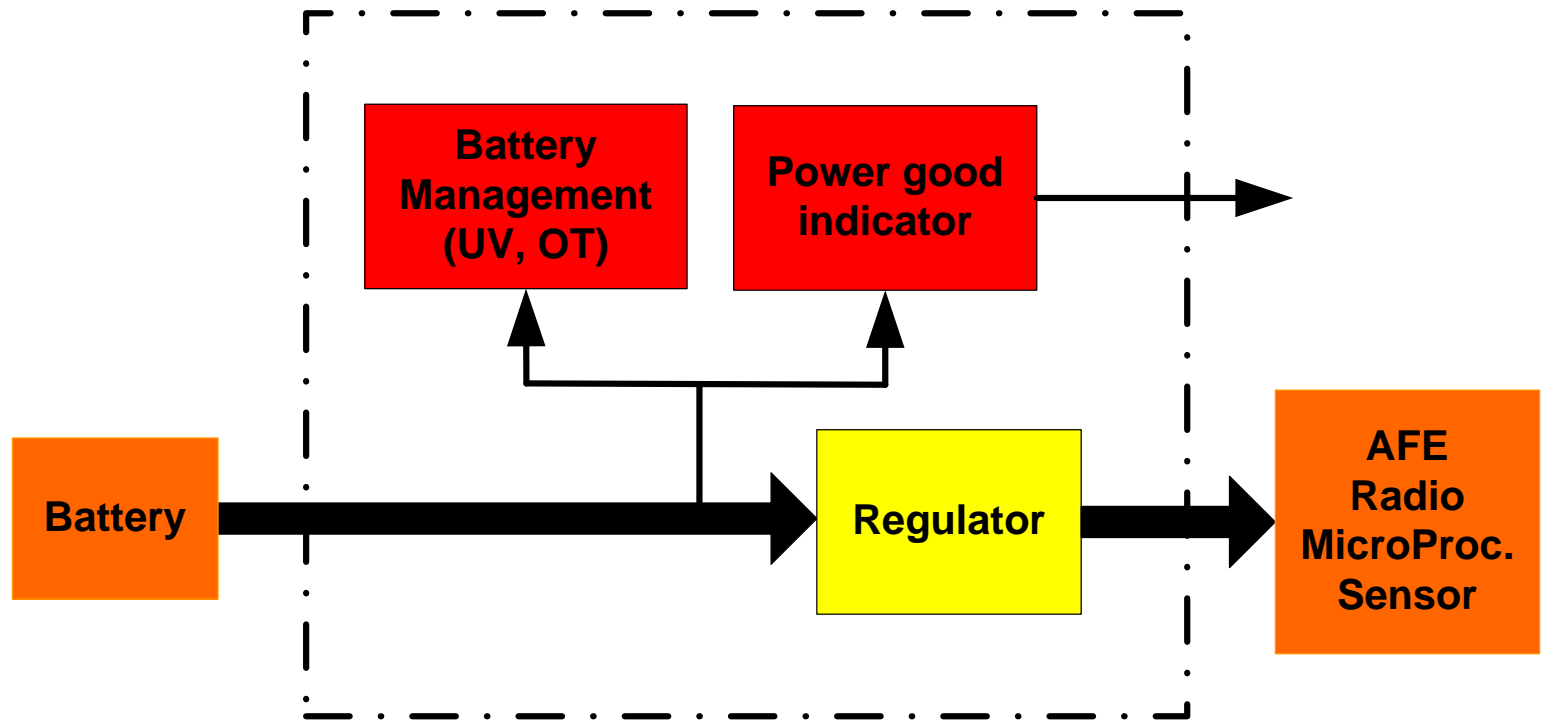


- Battery is an energy source
- System needs to be ON only when the load demands it

1cm³ Li-ion → 2800J → 1year at 100μW


Self-powered solutions desirable

Energy Harvesting System

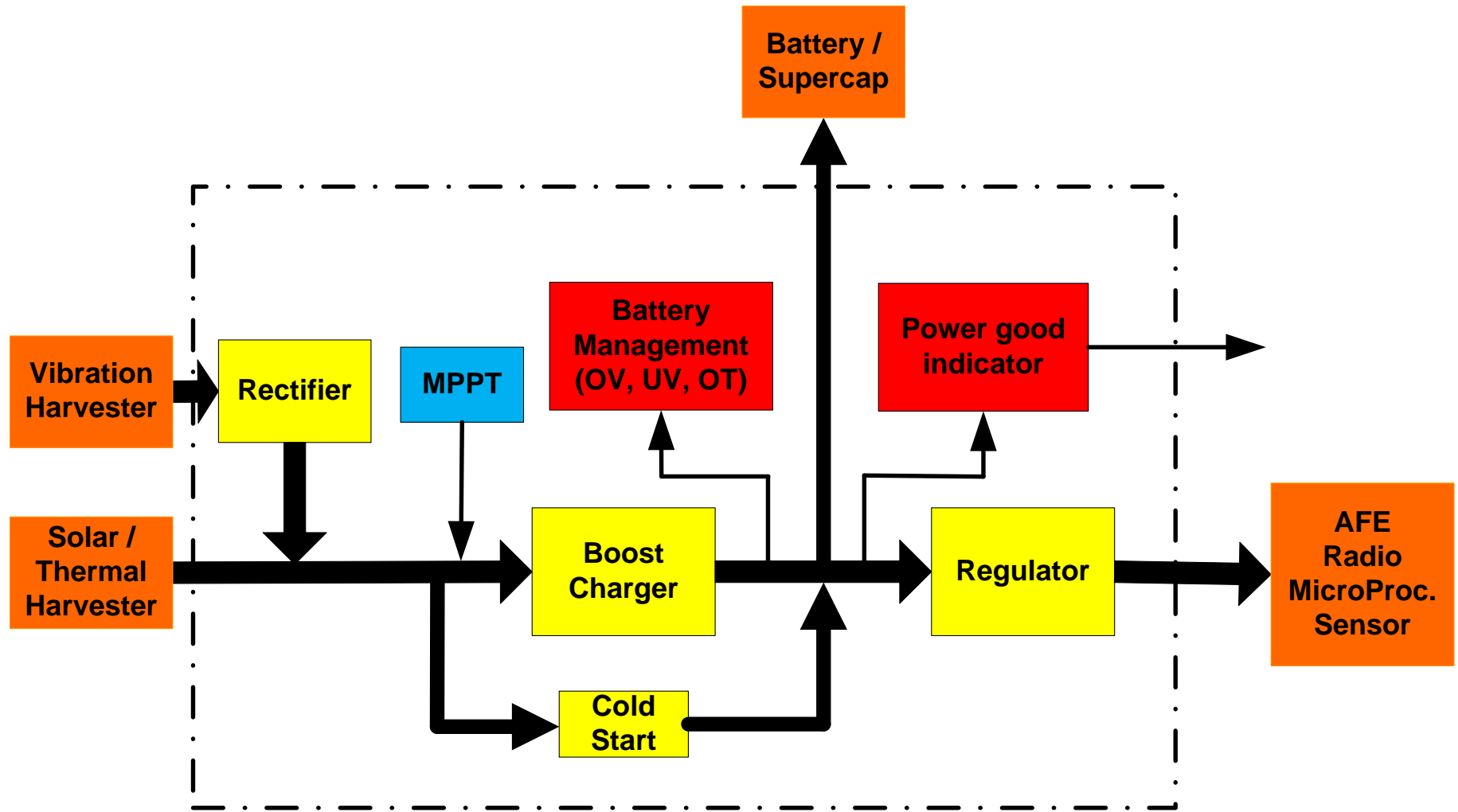


Energy harvesters are power sources

Harvesting Light Energy

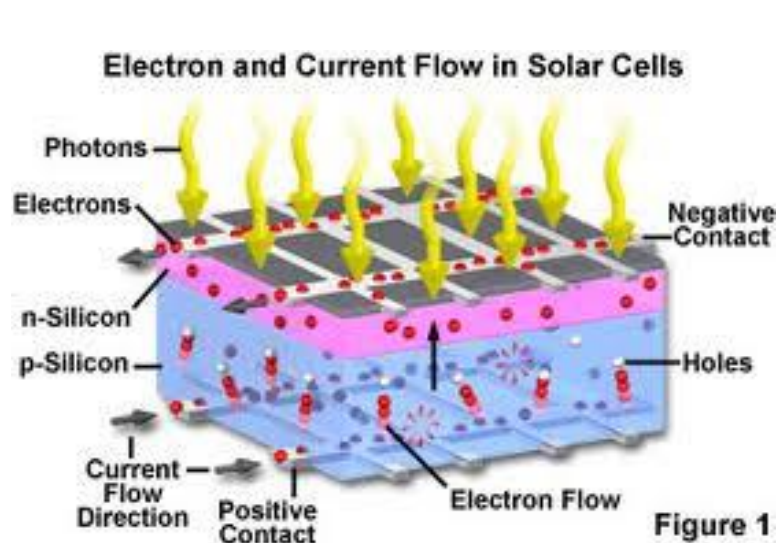


*US Department of Energy

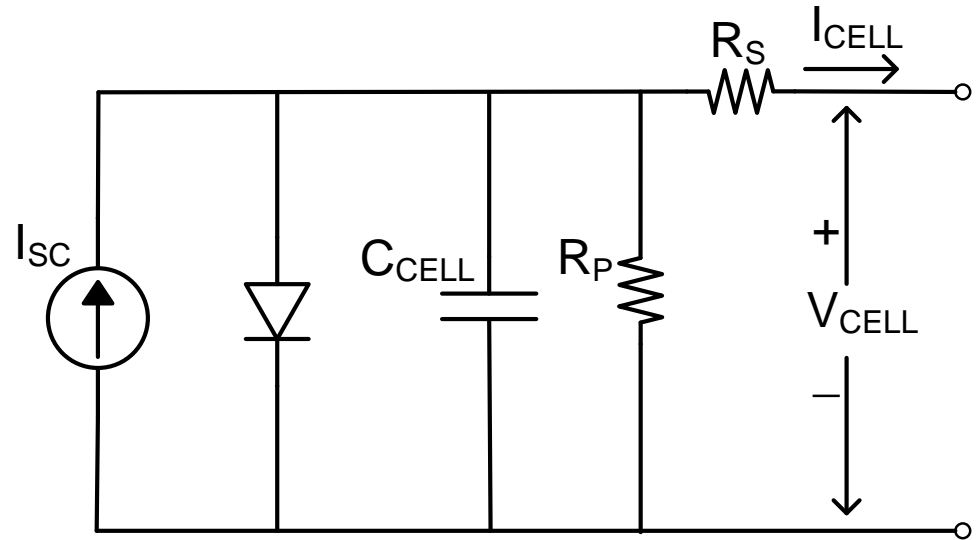


- Incident light generates electron-hole pairs
- I_{SC} proportional to light intensity
- Solar cell can be modeled as current source into a diode


I-V curves with light intensity

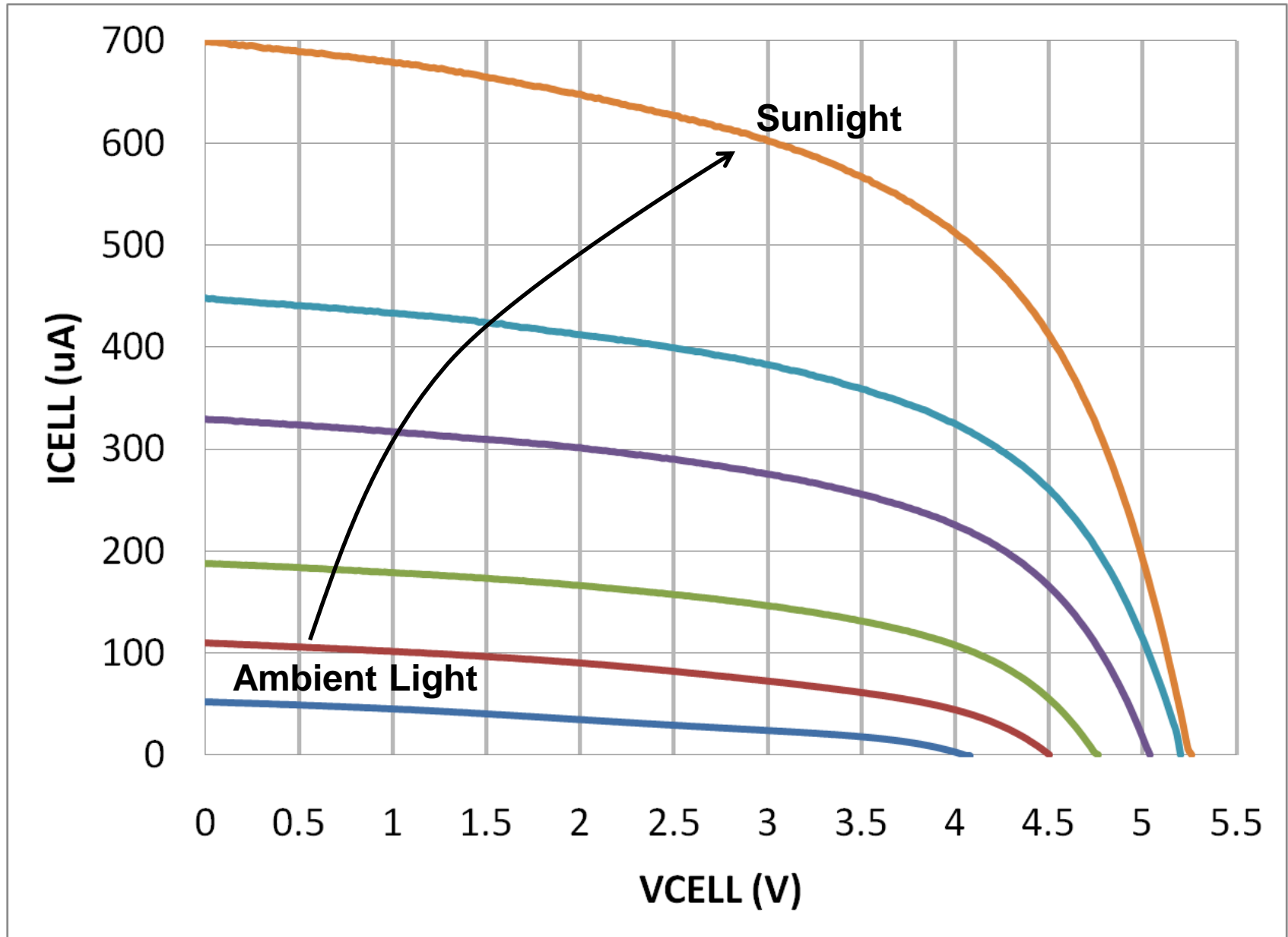

Output power curves with light intensity

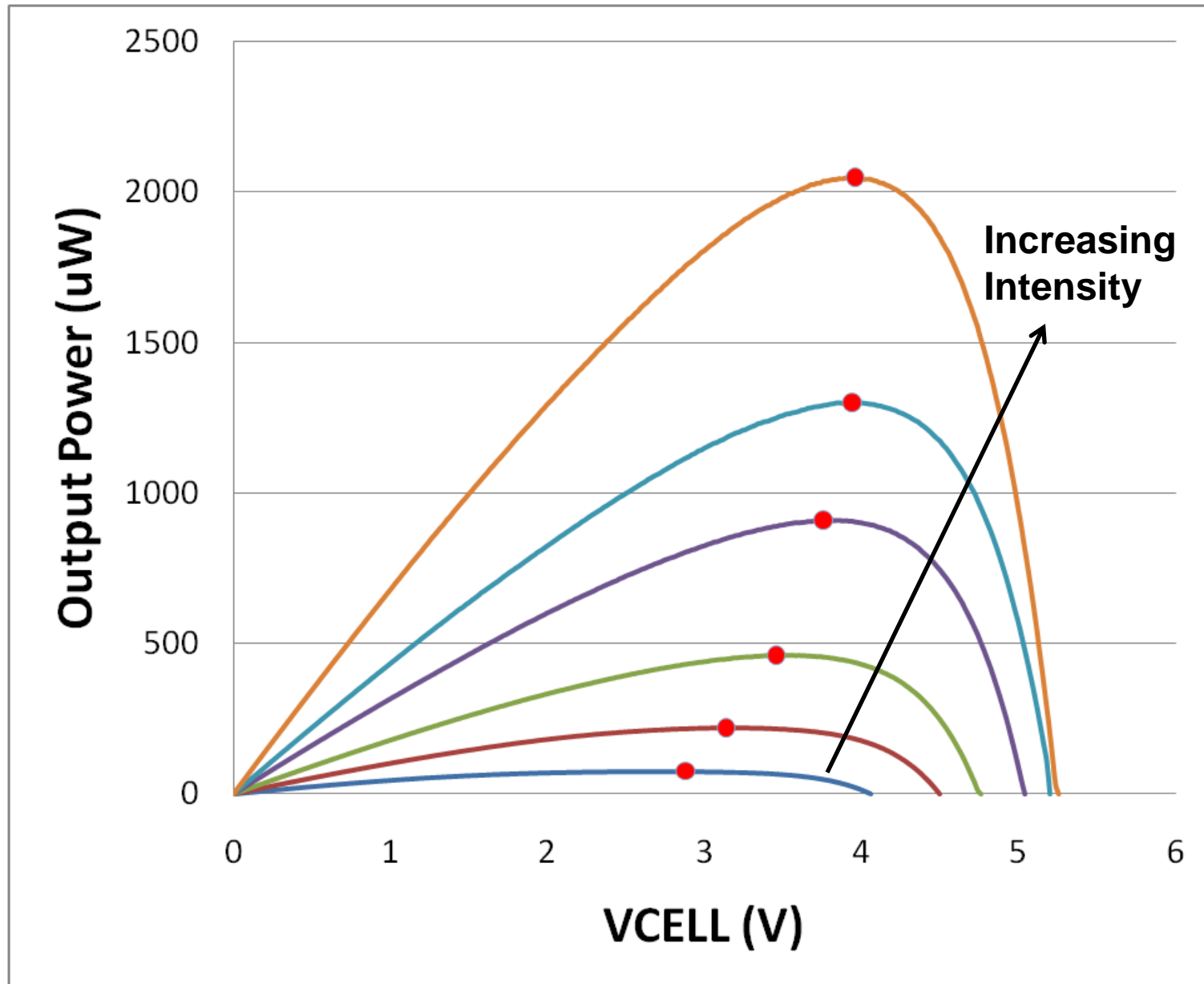


Thermoelectric Energy Harvesters

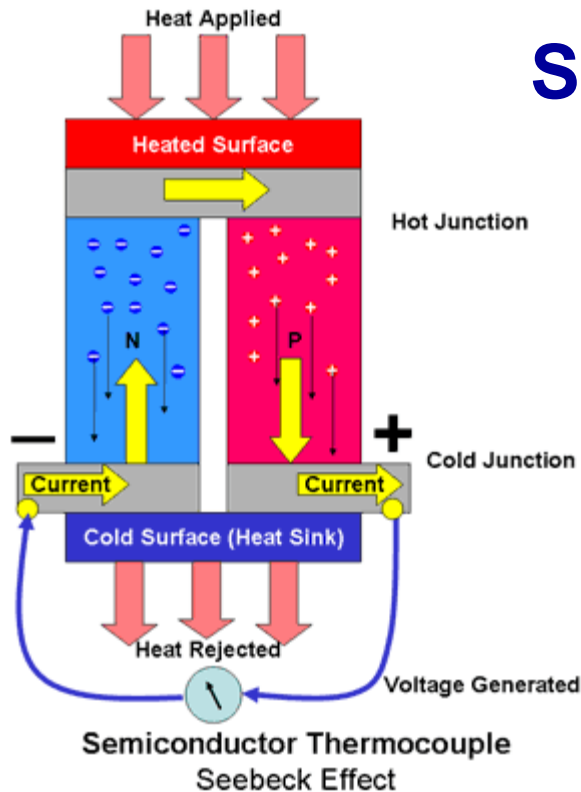

Seebeck Effect

[Micropelt]


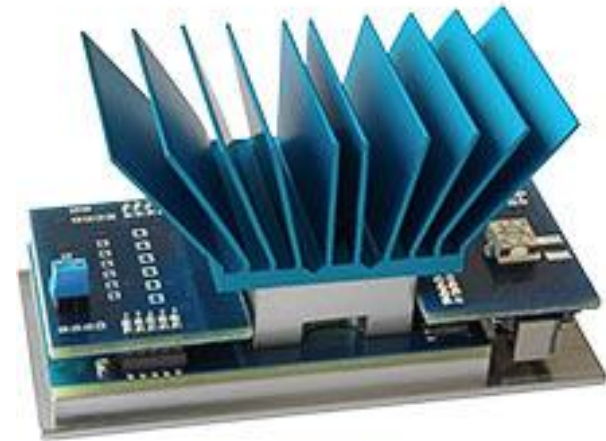


- Convert heat energy to electrical energy
- Bismuth Telluride preferred due to superior thermal properties
- One p-n leg generates $\sim 0.2\text{mV/K}$

Equivalent Circuit of Thermal Harvester

$$V_T = S\Delta T$$


Lim, Nasa Tech Briefs, 2008

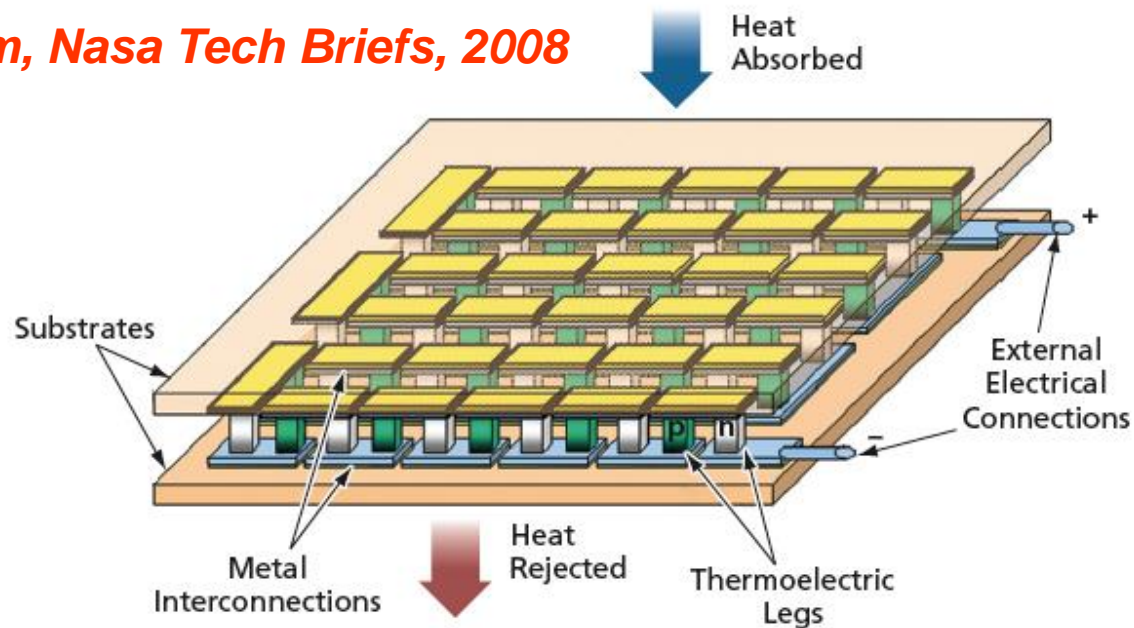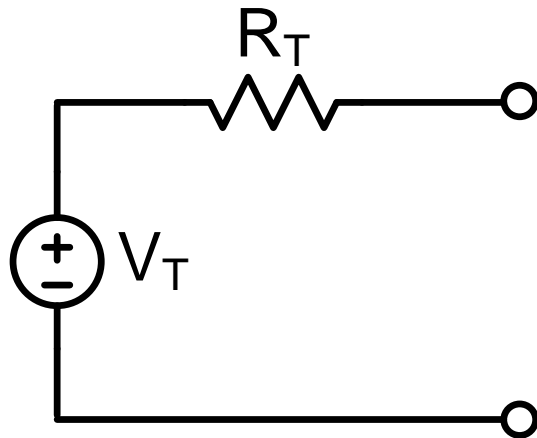


- Electrically in series, Thermally in parallel
- Open-circuit voltage proportional to temperature difference across TEG

TEG Characteristics

Open-Circuit Voltage

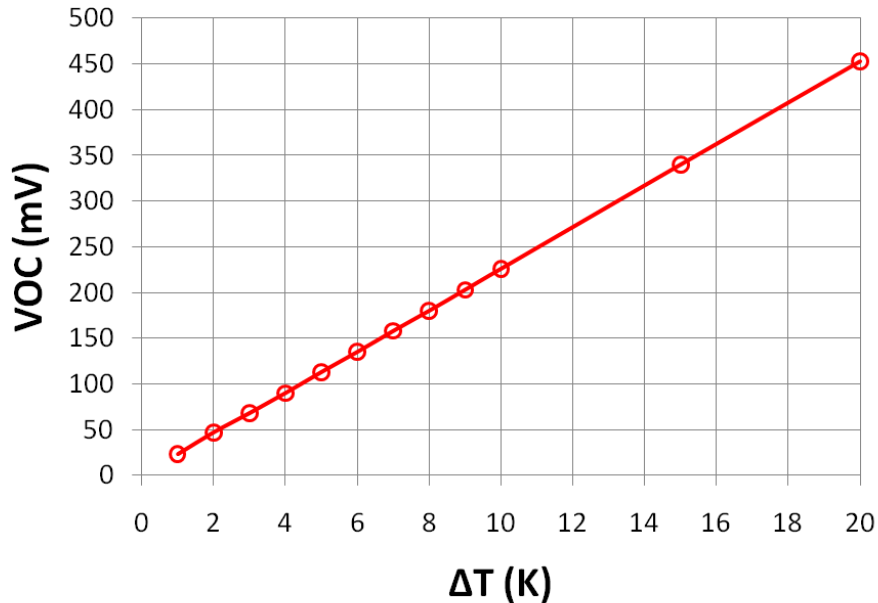


Maximum Power Output

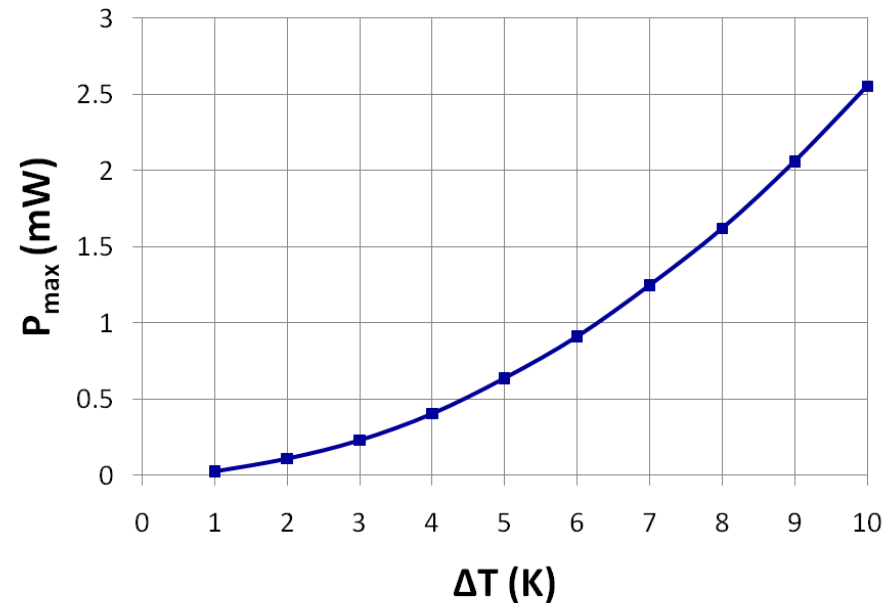


- Tellurex G1-1.0-127-1.27
- $S = 23\text{mV/K}$; $R_T = 5\Omega$
- <http://www.tellurex.com/power modules/p127.html>

[Tellurex]

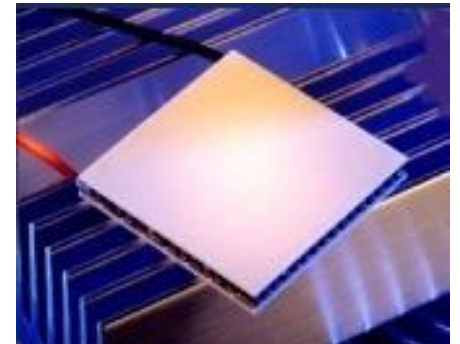


TEG Characteristics

Open-Circuit Voltage

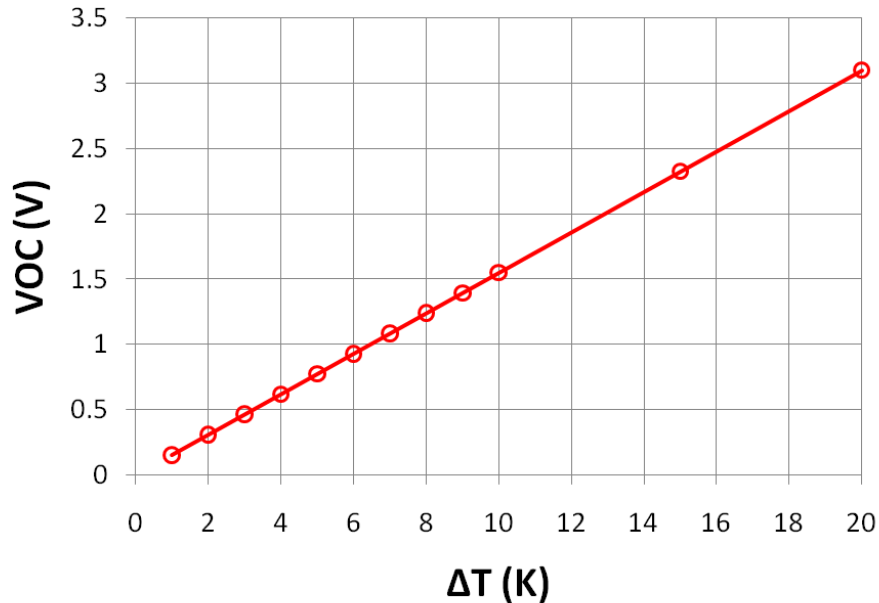


Maximum Power Output

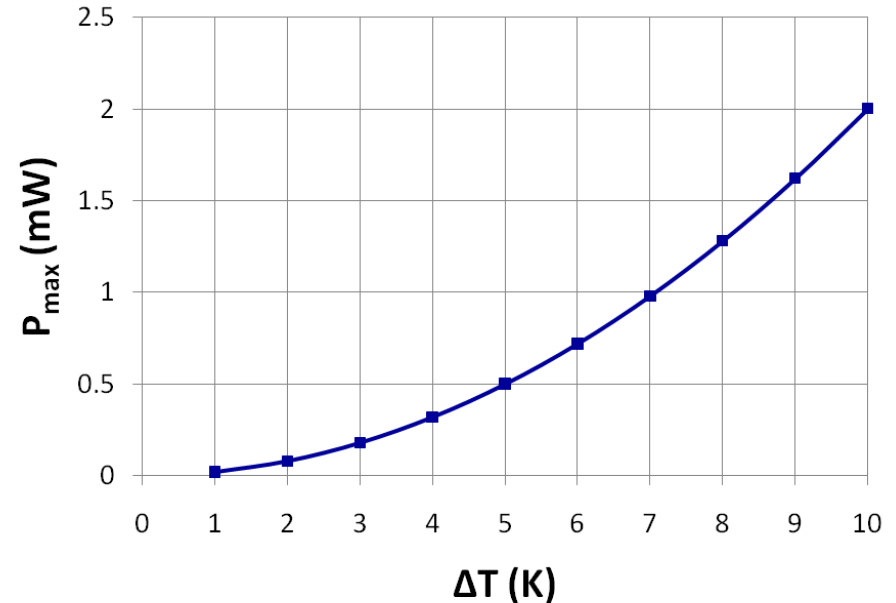


- Micropelt MPG-D751
- $S = 155\text{mV/K}$; $R_T = 300\Omega$
- <http://micropelt.com/products/thermogenerator.php>

[Micropelt]

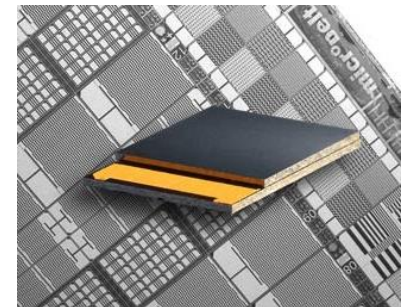


Body Heat Powered Electronics


System Concept

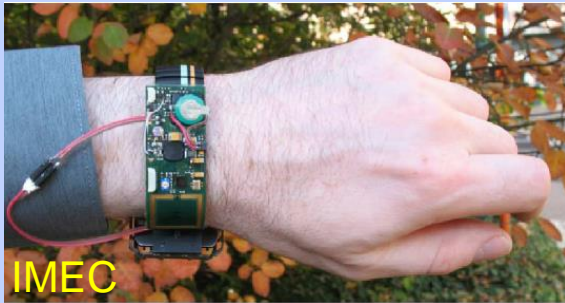

Thermo-Electric Devices

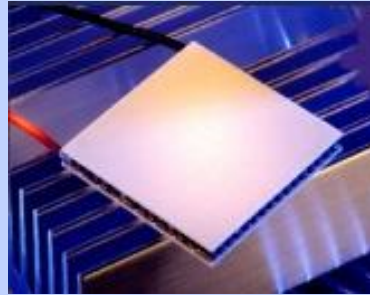


Tellurex

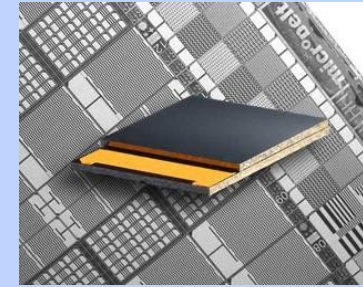


Micro-pelt

Thermal Energy Chip

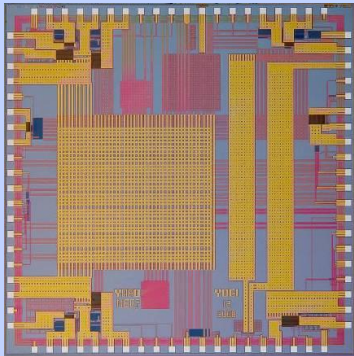


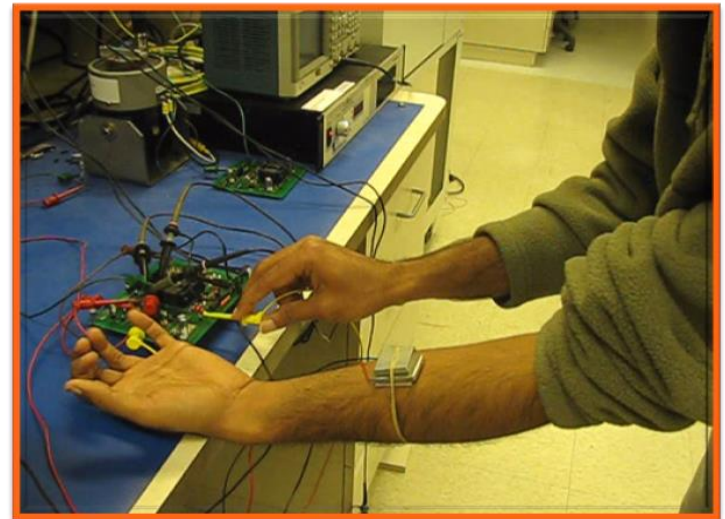[Y. Ramadass and A. Chandrakasan, ISSCC 2010]




For low-power wearable electronics

Electromagnetic Vibration Harvesters

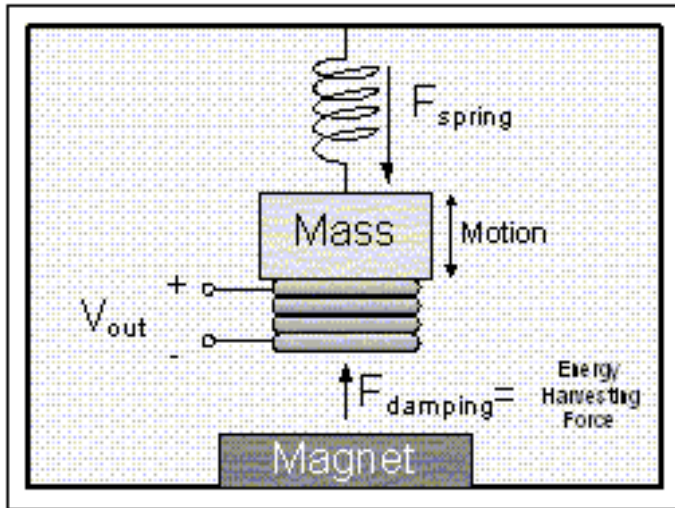

Simple equivalent circuit at resonance

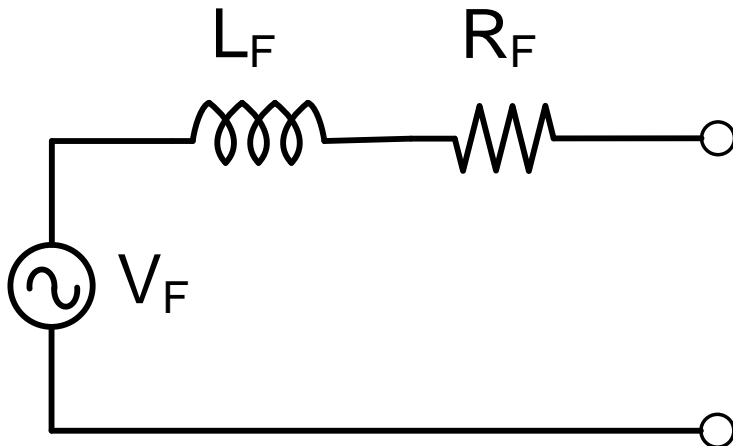


[Perpetuum]




[FerroSolutions]

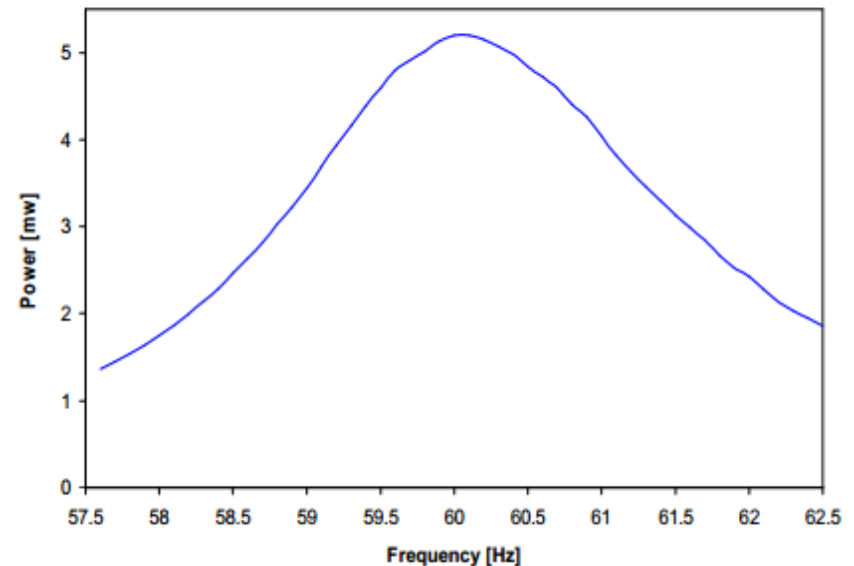Rectified DC Power at 100 mg into 50k Load



FerroSolutions VEH-460


Piezoelectric Vibration Harvesters

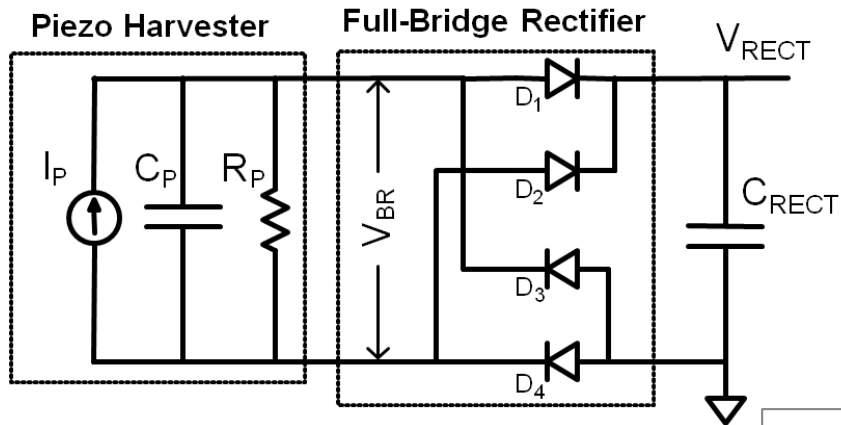

Mide Voltage v22b


- $V_P = 2.3V$
- $C_P = 12nF$
- $f = 225Hz$

Y. Ramadass, ISSCC, 2009

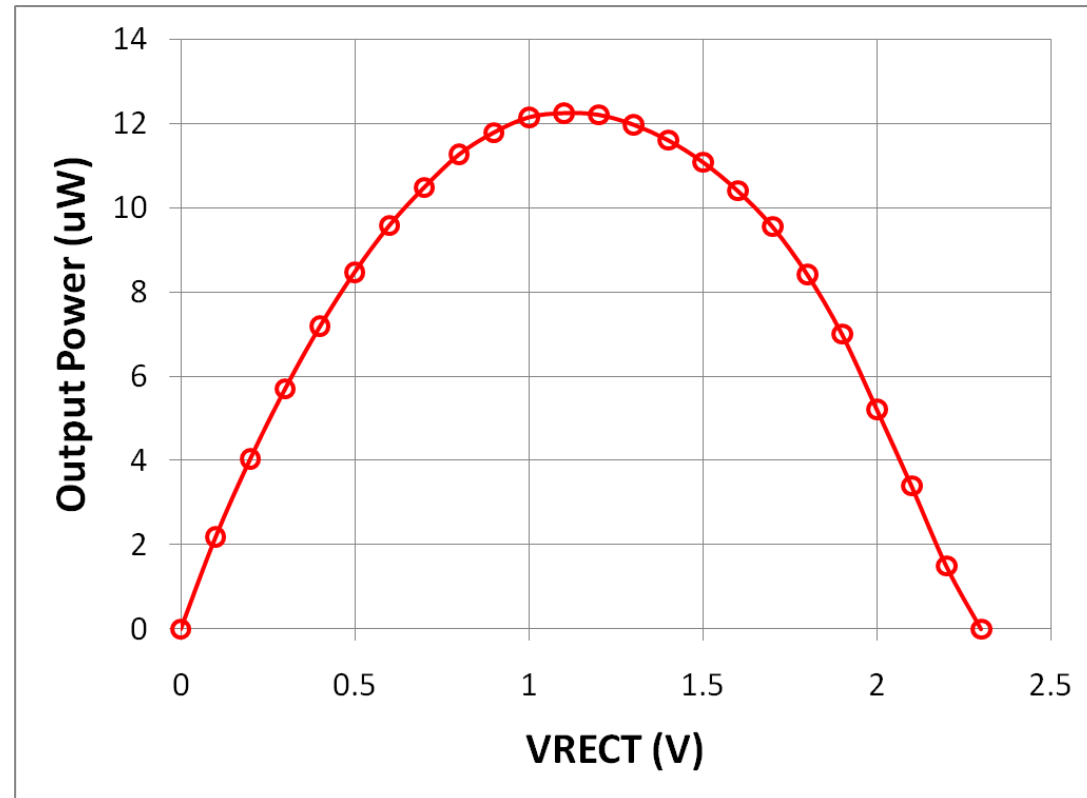


Vibration-to-Electric Energy

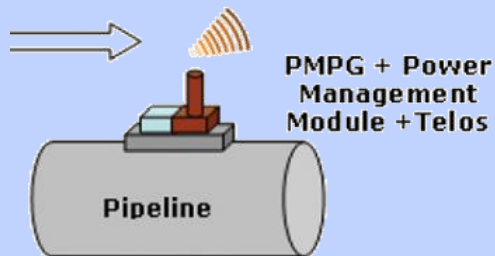Self-powered Wireless Corrosion Monitoring Sensors




Piezoelectric Micro-Power Generators

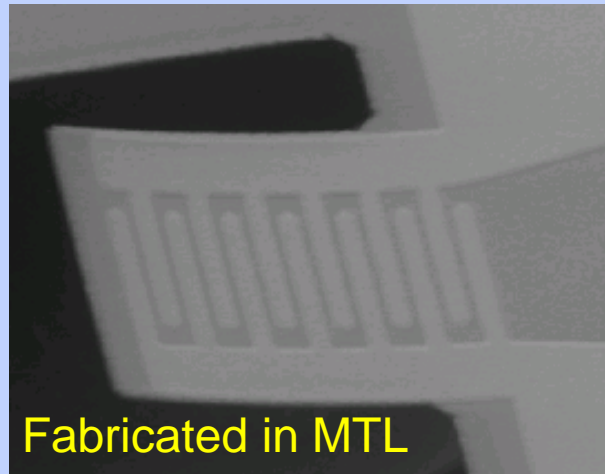

Sang-Gook Kim (MIT)

10 μ W -100 μ W generated

Power Converter

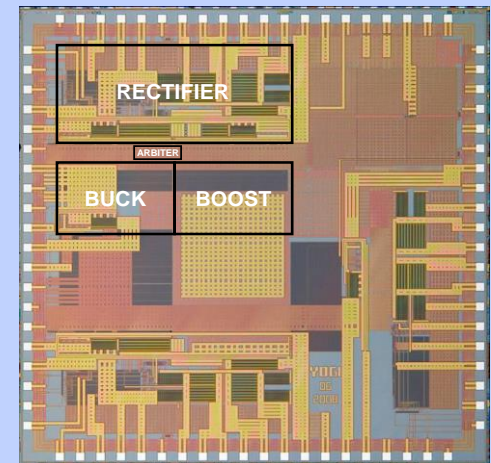

Vibrations Power Distributed Sensor Devices
(Battery-less Operation)


Energy Harvesting Sources

Energy Source	Characteristics	Efficiency	Harvested Power
Light	Outdoor	10~24%	10 mW/cm ²
	Indoor		10 μ W/cm ²
Thermal	Human	~0.1%	60 μ W/cm ²
	Industrial	~3%	~1-10 mW/cm ²
Wireless	Near field	> 60%	1-10 mW/cm ²
	Far field	< 1%	<10 μ W/cm ²
Vibration	~Hz–human	25~50%	~4 μ W/cm ³
	~kHz–machines		~800 μ W/cm ³

Seiko watch
~5 μ W




Holst Center
~40 μ W

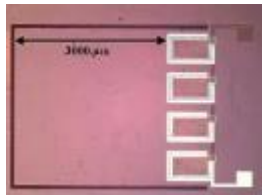

2 channel EEG
~1mW



AdaptivEnergy
~10mW

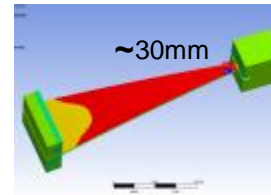

Elastometer
~800mW



BigBelly
~40W



1 μ W

10 μ W

100 μ W


1mW

10mW

100mW


1W+

Energy Storage Options

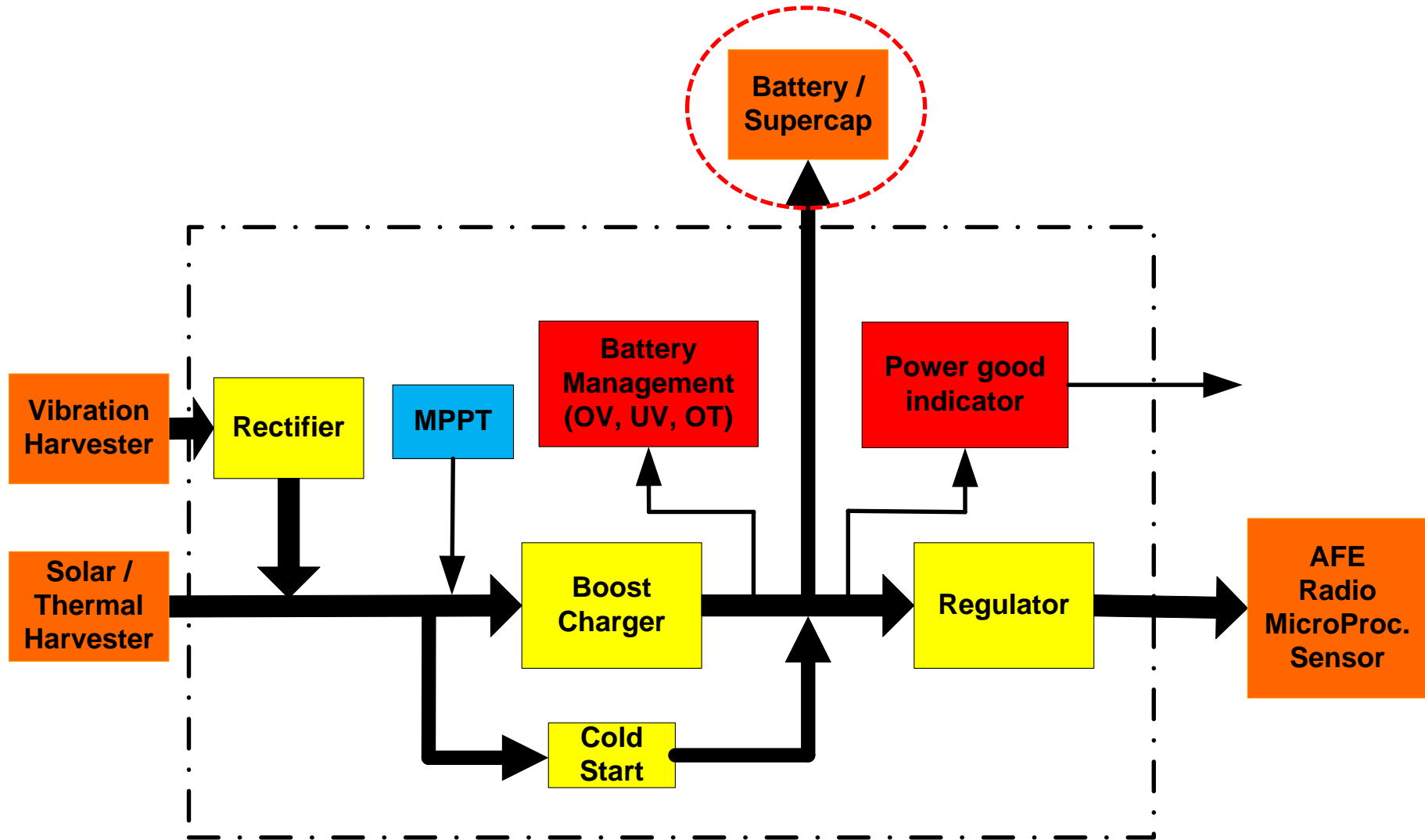


Store extracted energy from harvesters and provide to load

Energy Buffer

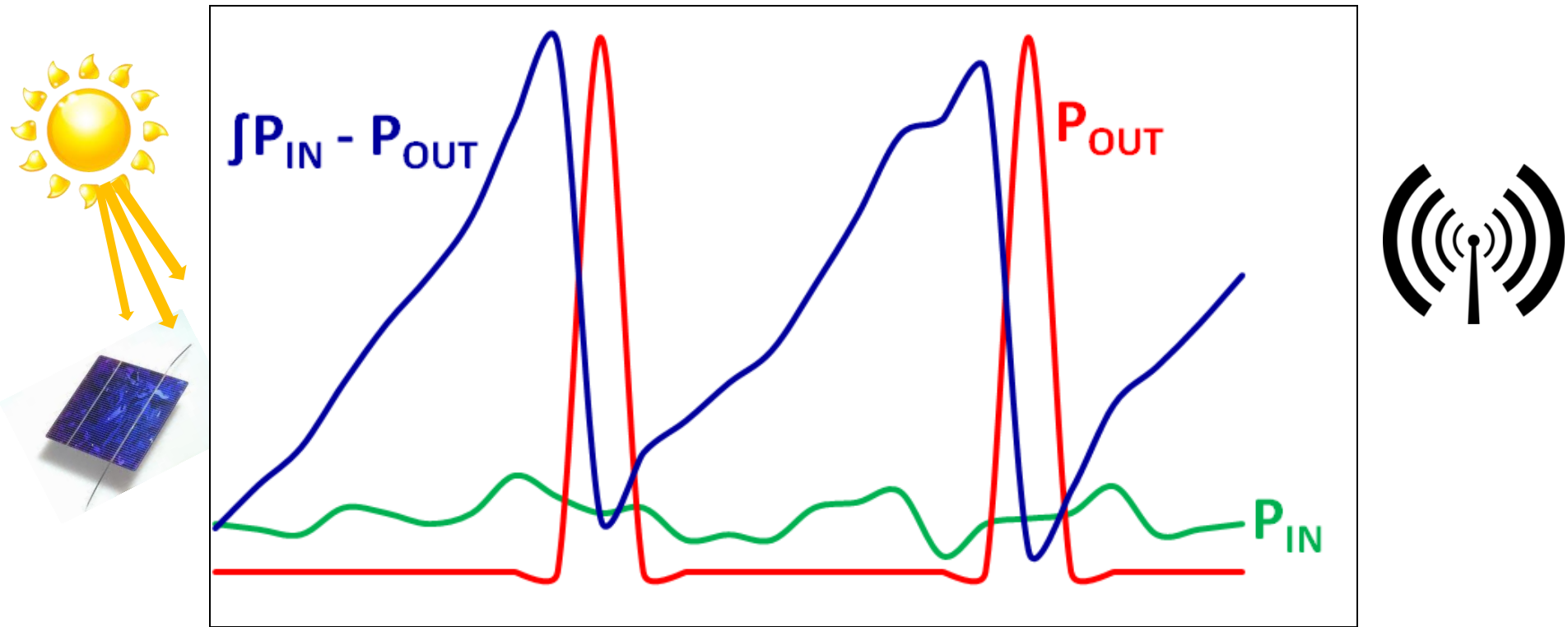

- Accumulate input power
- Provide peak output power
- Smooth out input, output power imbalances

Duty Cycle Impact on Current

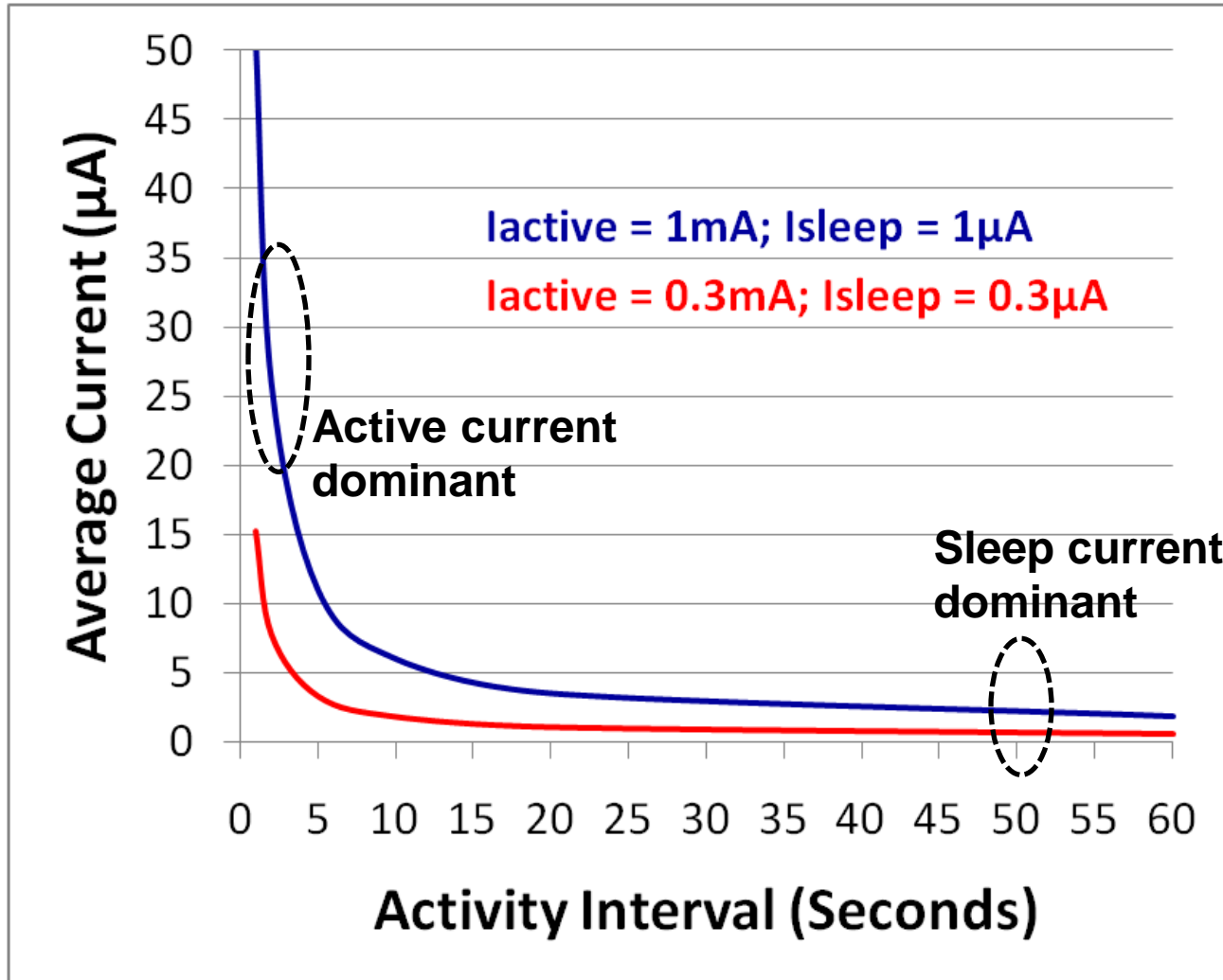


Pulse Width = 50ms

$$D = \frac{\text{Pulse Width}}{\text{Activity Interval}}$$

$$I(\text{avg}) = I_{\text{active}} * D + I_{\text{sleep}} * (1 - D)$$

Energy Storage Options


	Conventional Batteries
Recharge Cycles	100s
Self Discharge	Moderate
Charge Time	Hours
Impedance	Low - High
Physical Size	Large
Capacity	0.3-2500mAH

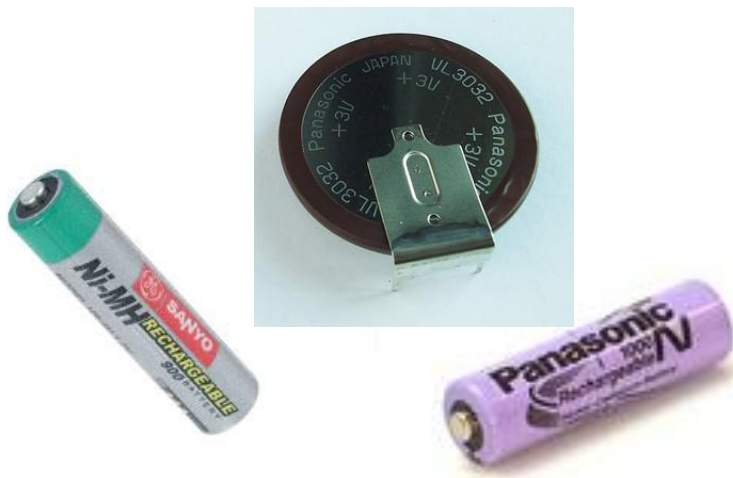

- NiCd, NiMH, Li chemistries
- AA, AAA batteries have high capacity, low internal impedance, higher self discharge
- Li coin cells have low capacity, high internal impedance, smaller form factor

Energy Storage Options

	Conventional Batteries	Thin Film Batteries
Recharge Cycles	100s	5k-10k
Self Discharge	Moderate	Negligible
Charge Time	Hours	Minutes
Impedance	Low - High	High
Physical Size	Large	Small
Capacity	0.3-2500mAh	12-2200 μ AH

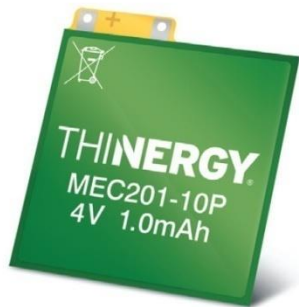

- Solid-state LiPON electrolyte
- Higher output currents compared to coin cells
- Extremely low self-discharge
- Variety of form factors, intrinsically safe, high temp.

Energy Storage Options


	Conventional Batteries	Thin Film Batteries	Supercaps
Recharge Cycles	100s	5k-10k	Millions
Self Discharge	Moderate	Negligible	High
Charge Time	Hours	Minutes	Sec-Minutes
Impedance	Low - High	High	Low
Physical Size	Large	Small	Medium
Capacity	0.3-2500mAH	12-2200 μ AH	10-100 μ AH

[AVX]



- Supports high peak output currents
- Very high leakage currents
- Wide range of operating temperature


Energy Processor

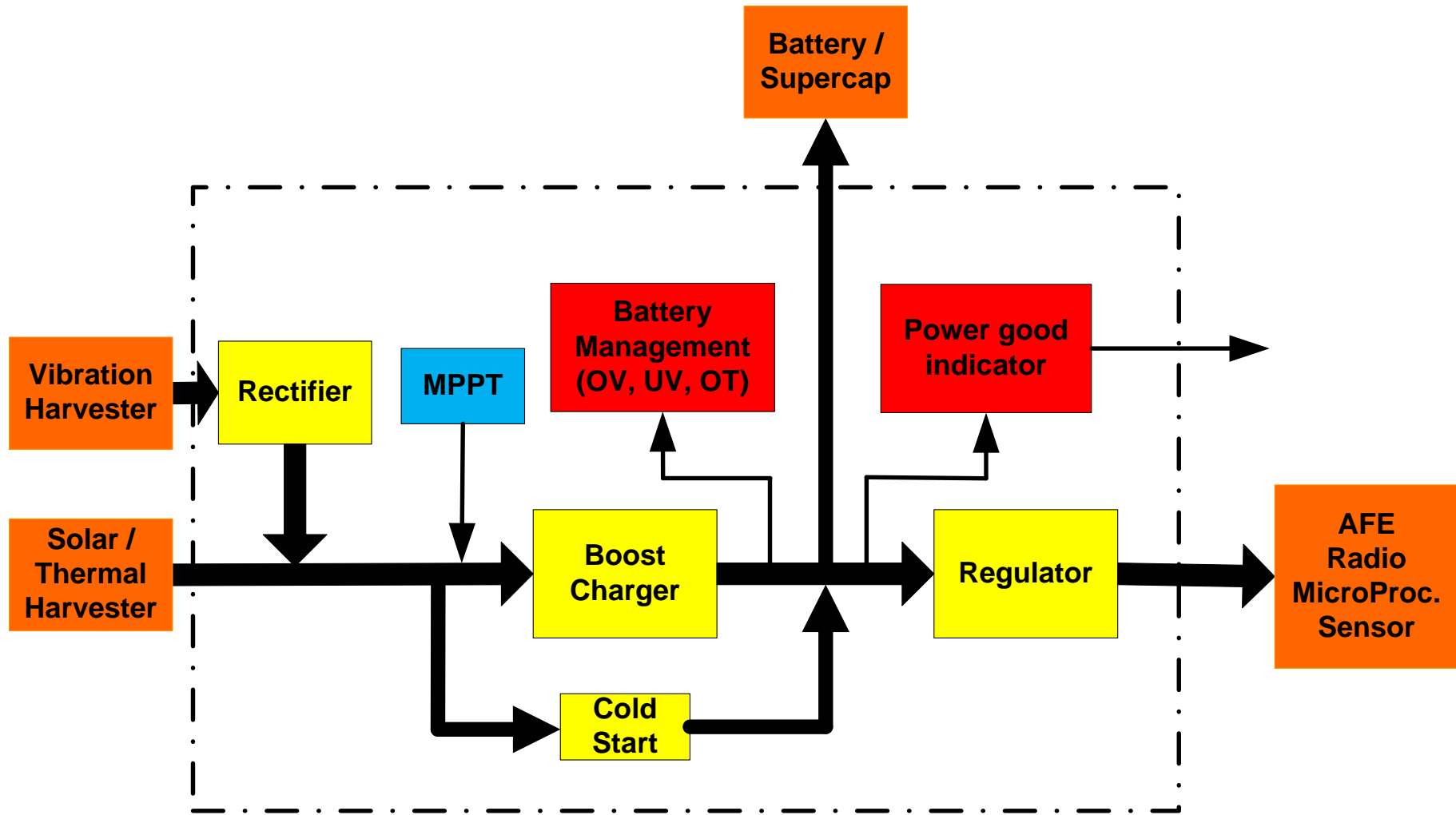


Take input energy from harvester and charge the storage element efficiently

Energy Mgmt. IC -BQ25570

<http://www.ti.com/product/bq25570>


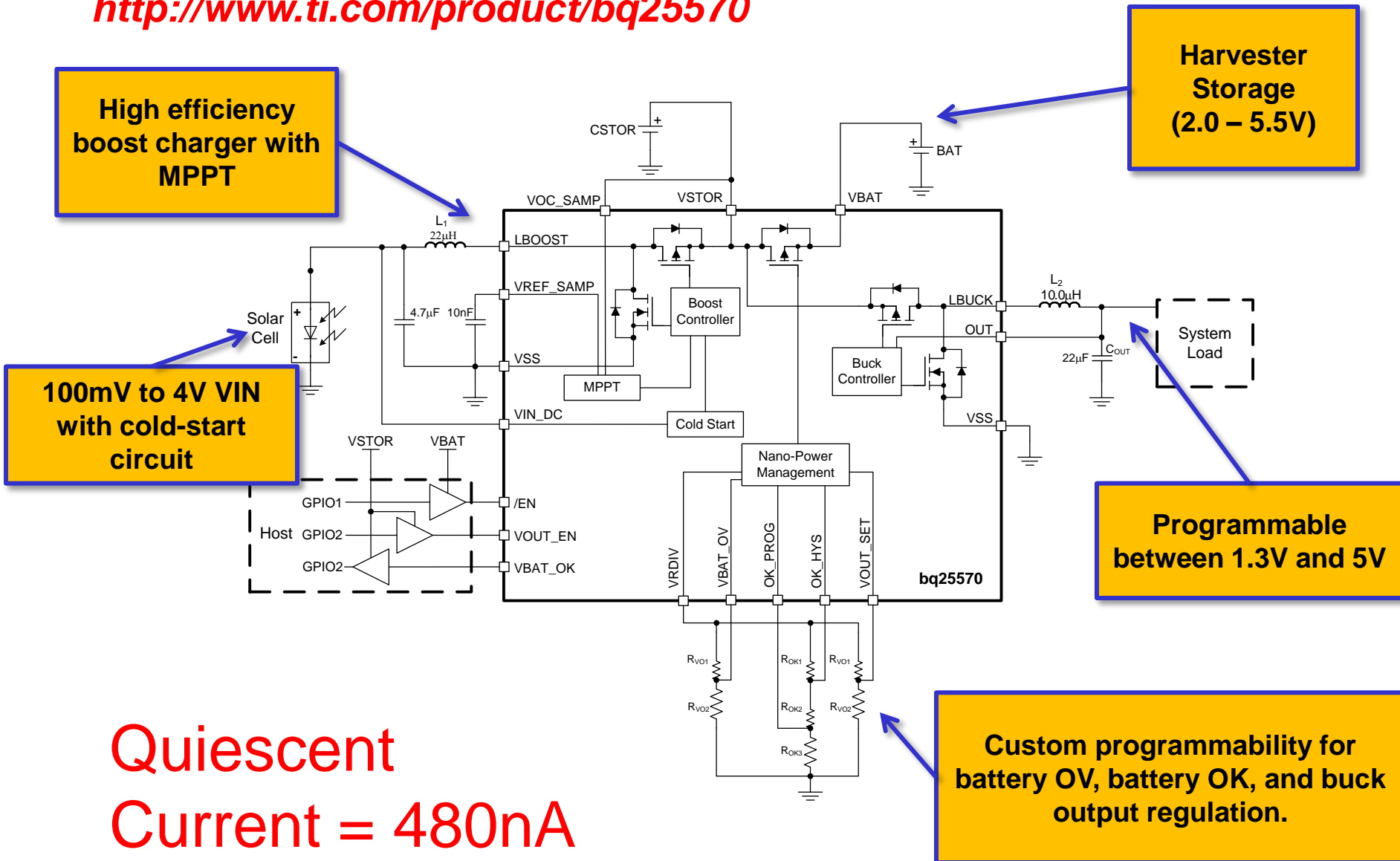


BQ25570 Charger Architecture

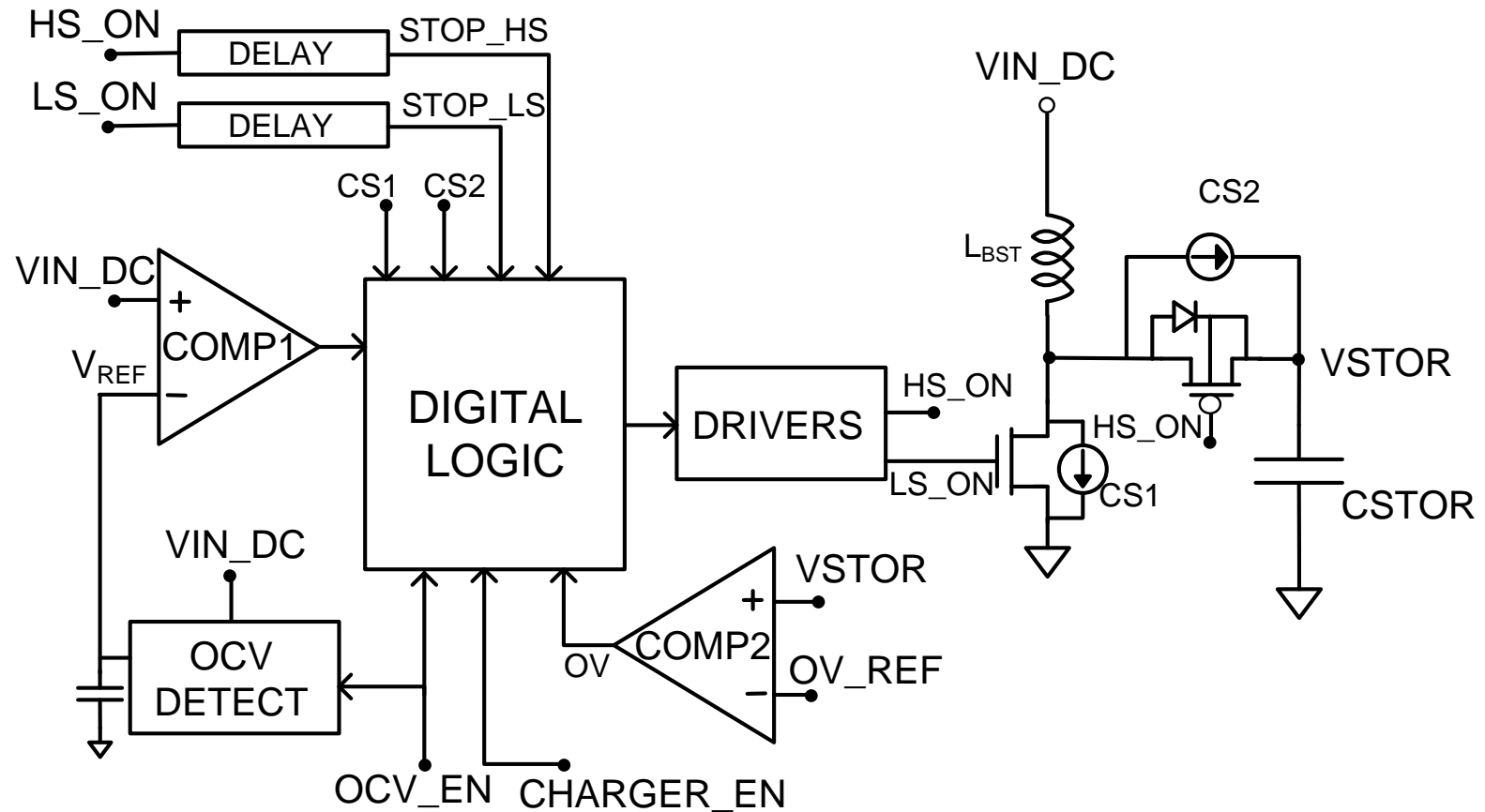

- Synchronous boost converter with input regulation
- 80mV – 4V input voltage
- 10 μ A – 100mA input current

Charger Operation

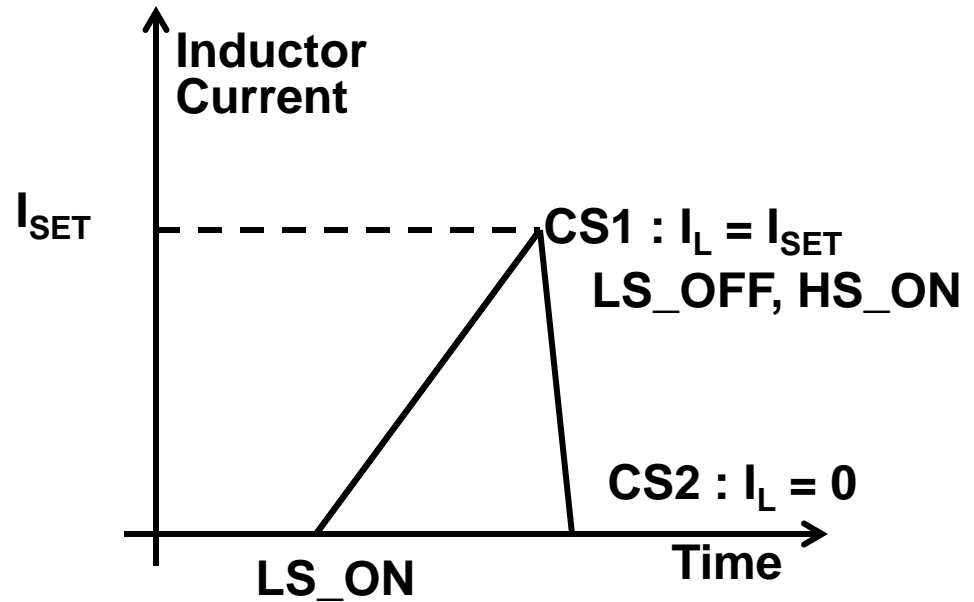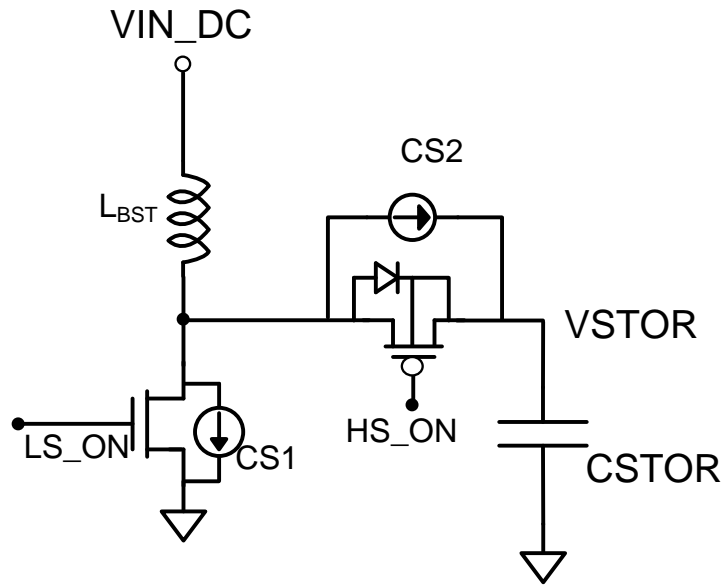


- When $VIN_DC > V_{REF}$
 - LS_ON = hi and LS_ON remains high till I_L hits I_{SET}
- Once CS1 goes high (i.e $I_L = I_{SET}$),
 - LS_ON = lo and HS_ON = hi
- HS_ON remains high till $I_L = 0$ (CS2 detects this)

BQ25570 Charger Efficiency


- **Single** cell solar operation in indoor light (200 lux)
- Harvesting from thermoelectric generators

Eff Vs I_{in}

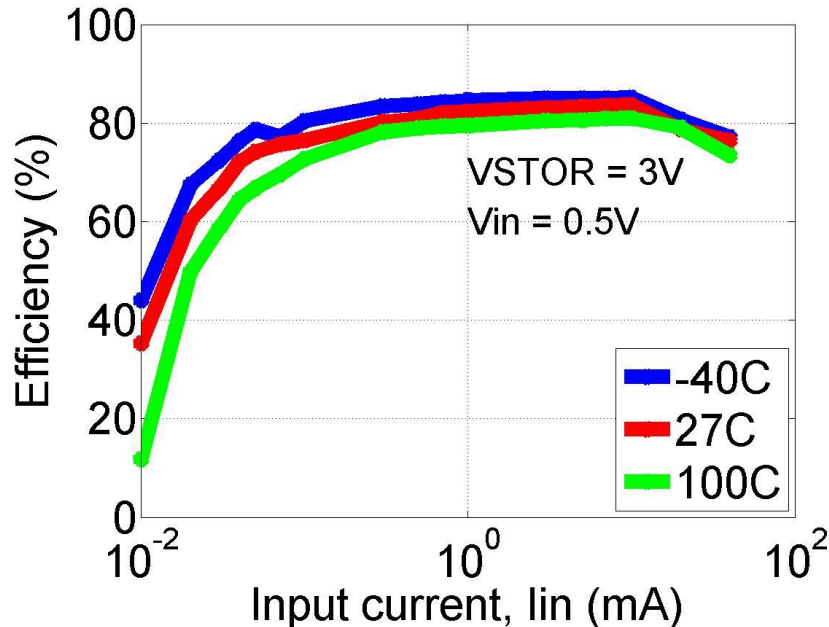


- 35% efficiency with 10 μ A input at 0.5V
- > 80% above 100 μ A.

Eff Vs V_{in}

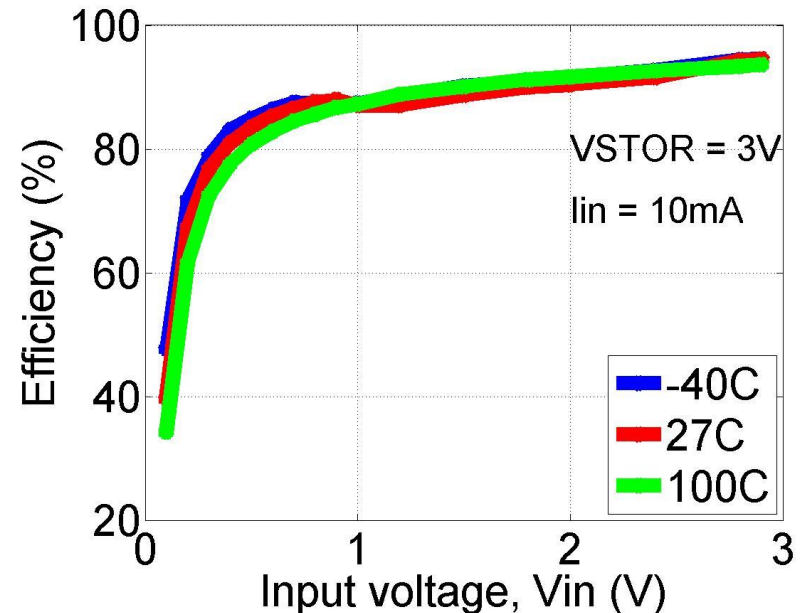



- 38% efficiency with 100mV input at 10mA
- >80% above 0.5V

Revisiting solar MPP curves

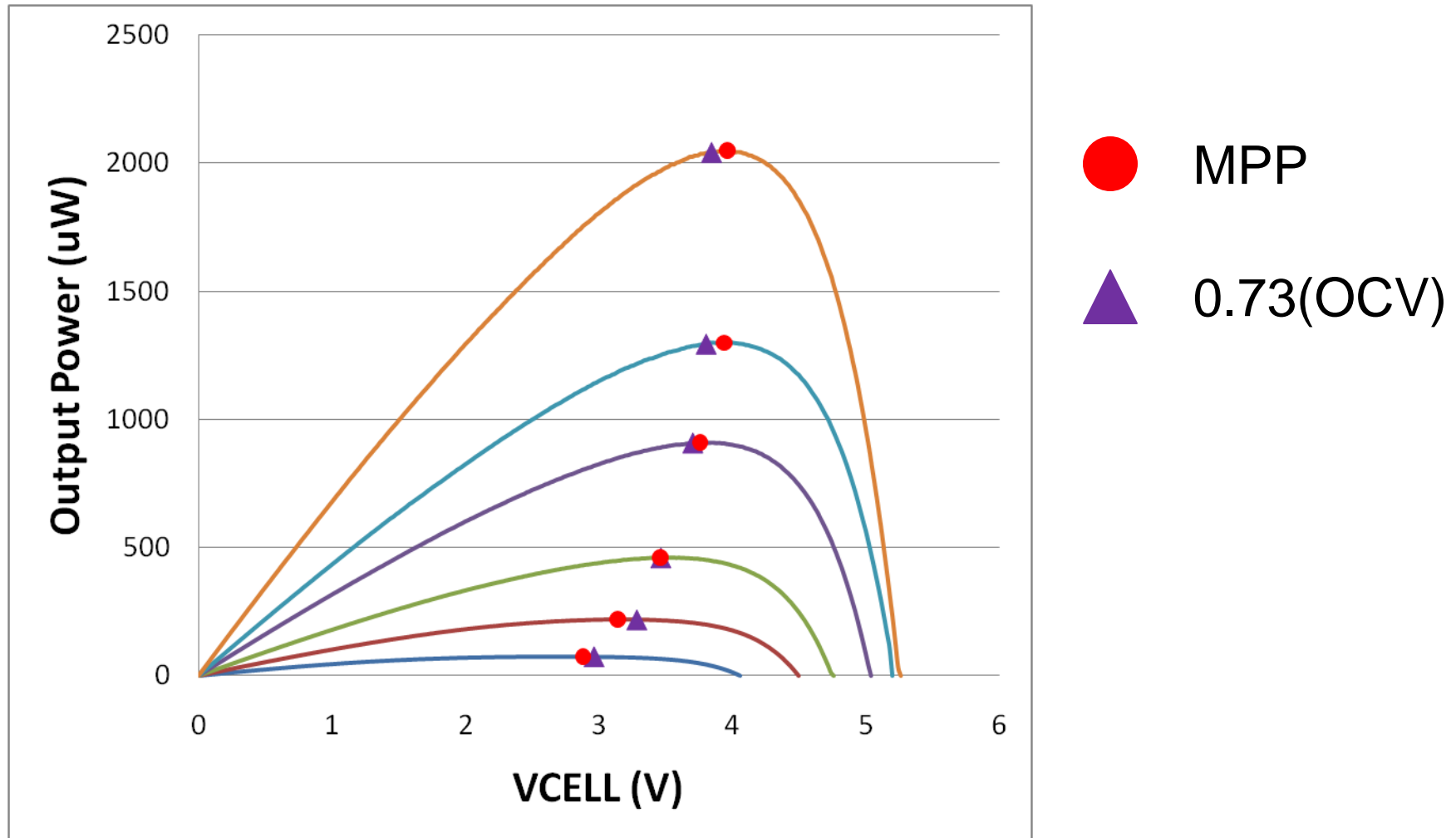

Output power levels within 0.5%


BQ25570 Maximum Power Point Tracking

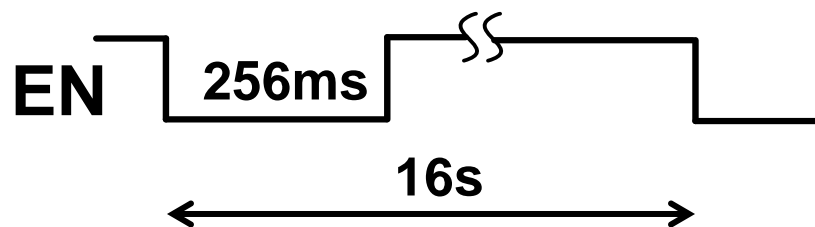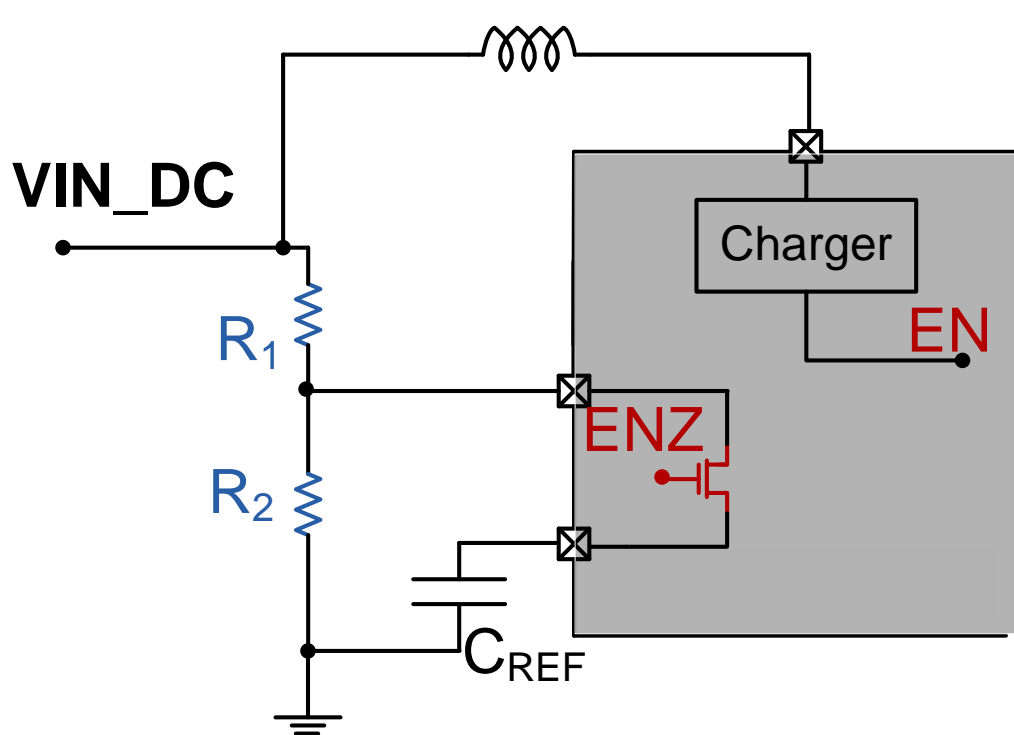

	Solar	TEG
MPPT fraction	~75%	50%


- Open circuit voltage based MPPT
- Charger periodically turned off using **EN** signal
- IC samples and holds fraction of OCV on external capacitor
- Charger regulates input to value held on capacitor

MPPT waveforms

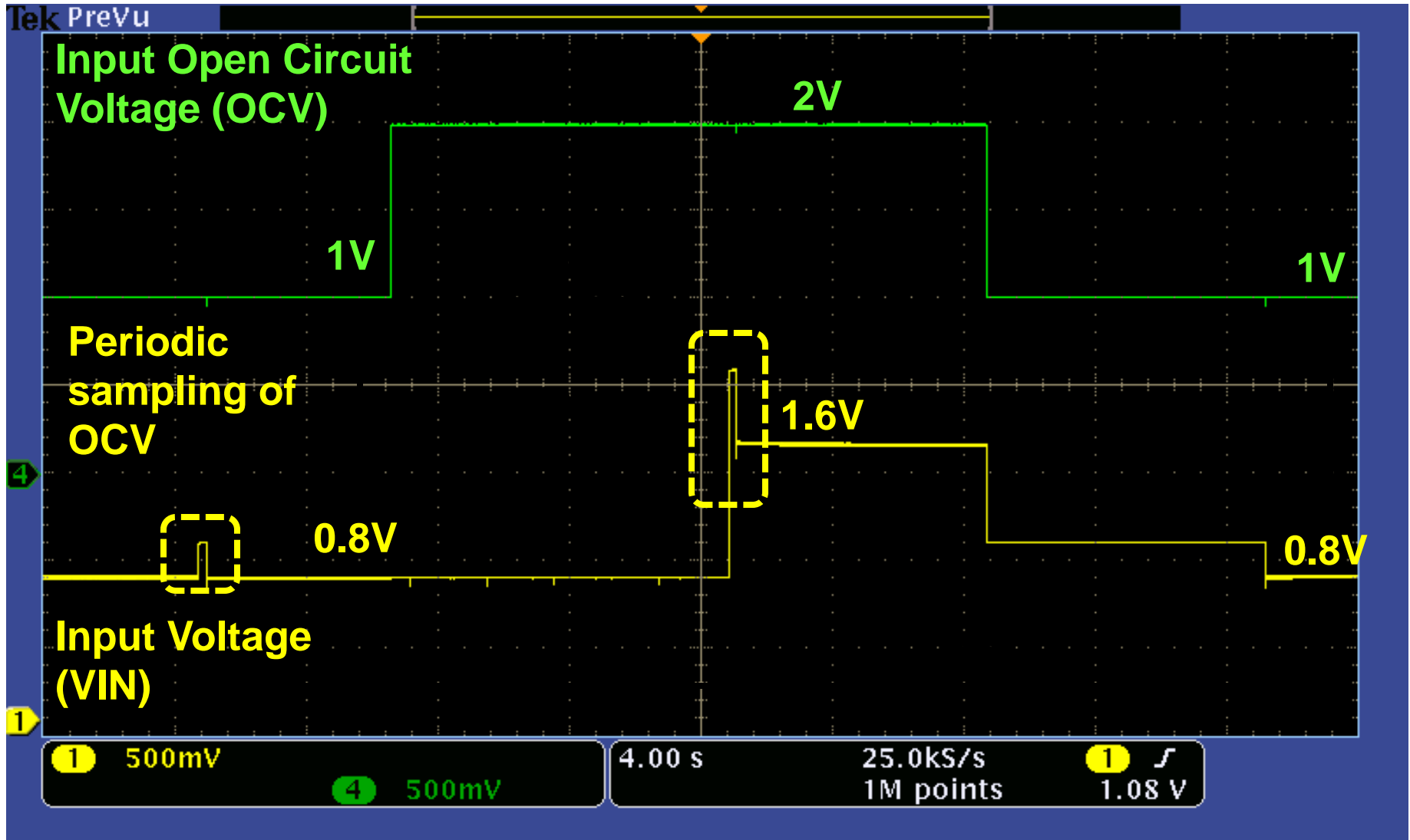


Cold Start

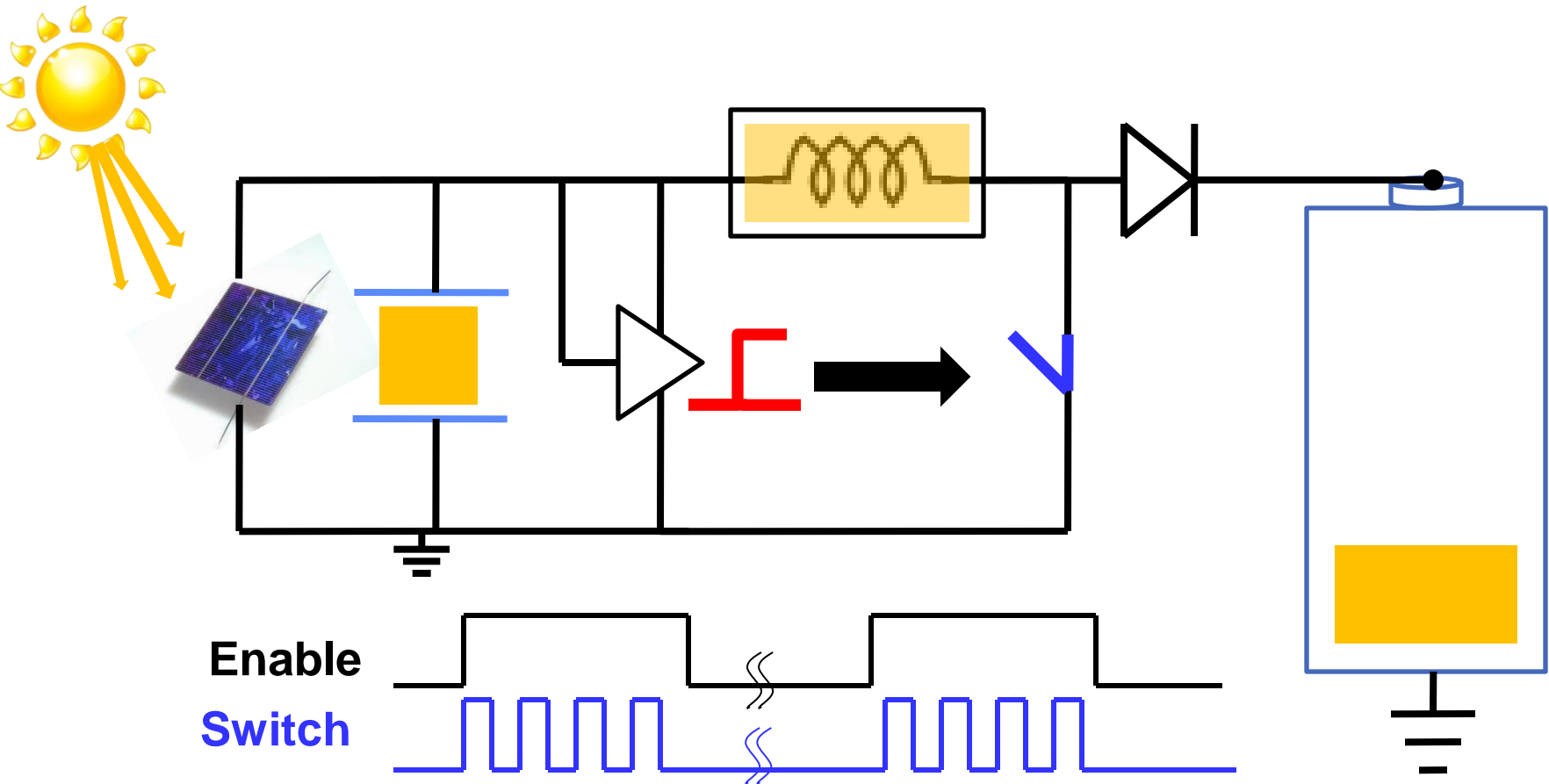- Function : Start system with depleted storage
- Architecture : **Input** powered boost converter




330mV Cold Start Circuit

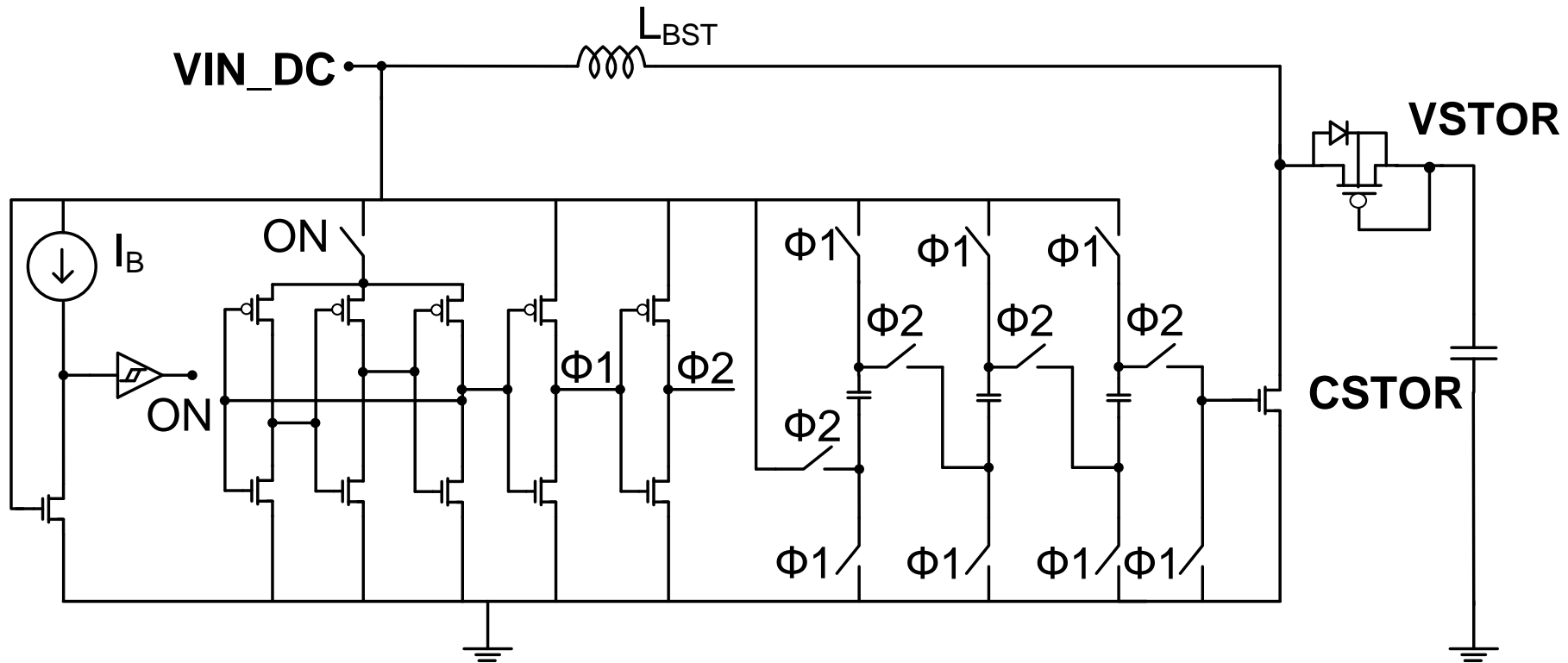

K. Kadirvel, ISSCC, 2012

- Low V_t low side switch
- Body diode of main charger high side switch


20mV Startup with Meissner Oscillator

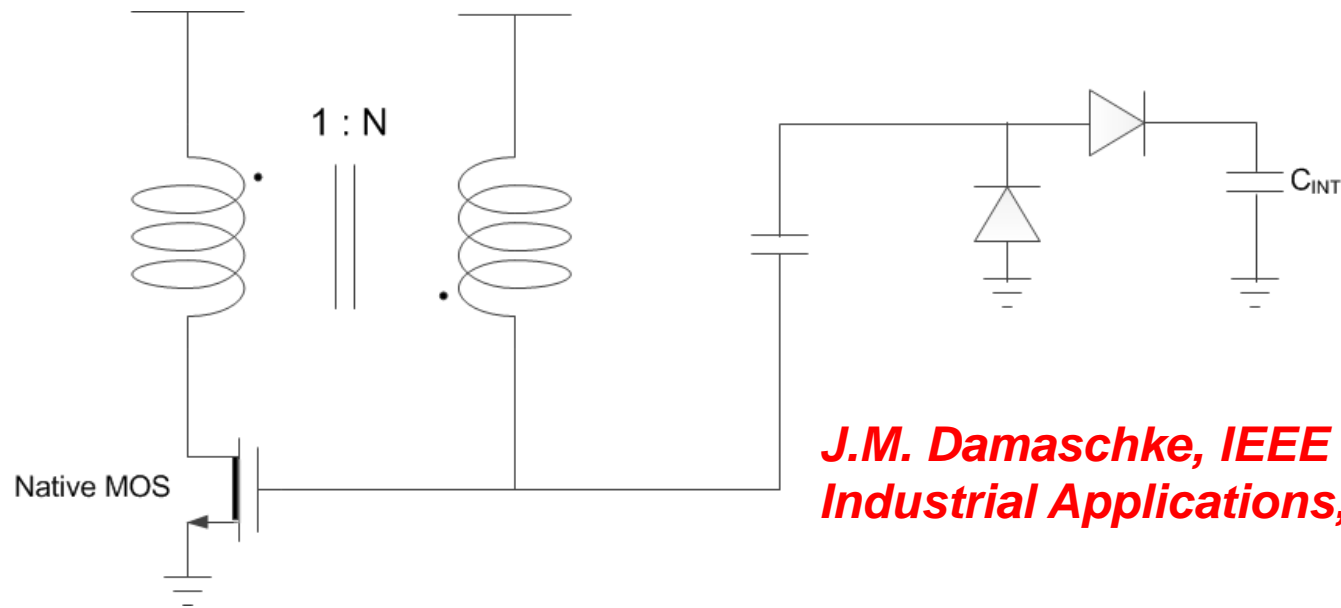

J.M. Damaschke, IEEE Trans. on Industrial Applications, 1997

- Oscillator frequency set by L_{sec} and C_{gs}
- Loop gain
 - Magnitude condition satisfied by transformer ($N \sim 20-100$)
 - Phase: 180° by common-source amplifier, 180° by transformer connection
- LTC3108, ECT310 use similar technique


Regulator

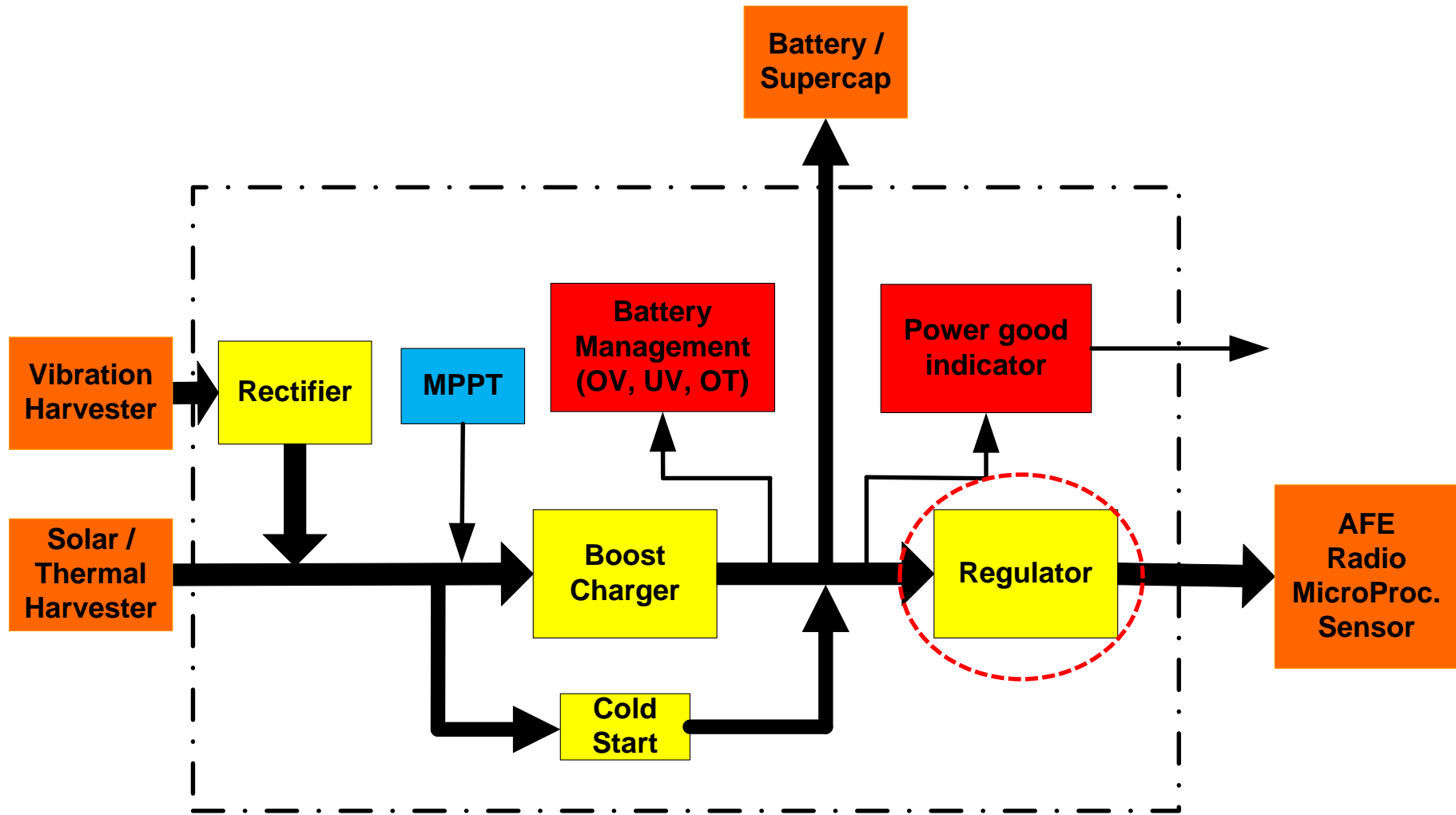

Present stored energy as a regulated supply to load circuits

DC-DC Converter Topologies

	Linear (LDO) Regulators		
Fully integrated	✓		
High efficiency	✗		
Voltage Scalability	✓		

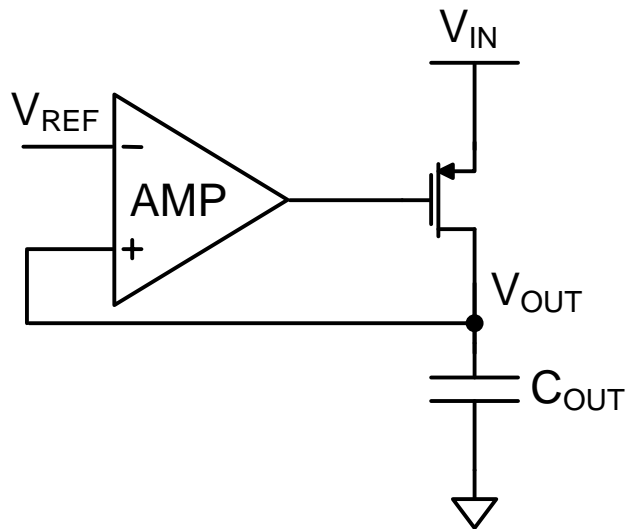


- Linear loss in efficiency
- Compact and easy to control

$$\eta = \frac{V_{OUT}}{V_{IN}}$$

M. Al-Shyoukh et al., "A Transient Enhanced Low-Quiescent Current Low-Dropout Regulator with Buffer Impedance Attenuation" IEEE JSSC, Aug 2007

DC-DC Converter Topologies

	Linear (LDO) Regulators	Switched Capacitor Converters	
Fully integrated	✓	✓	
High efficiency	✗	✓	
Voltage Scalability	✓	✗	

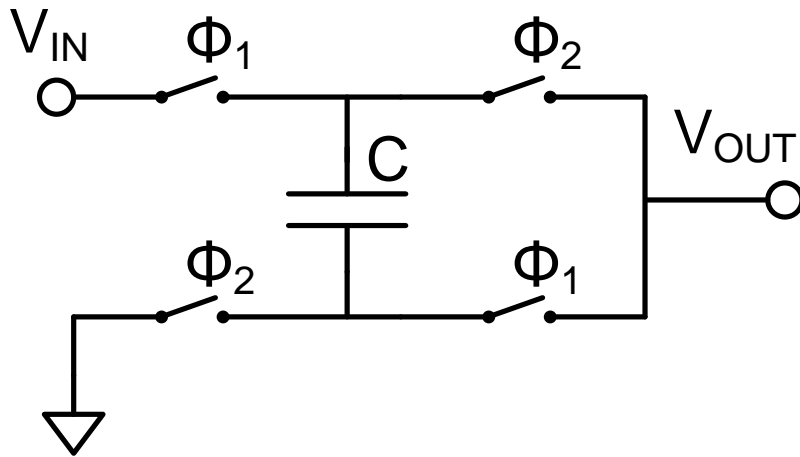


- Maintaining efficiency across load voltages is difficult
- Output current capability is limited

- 1) Y. Ramadass et al., "A 0.16mm² Completely On-Chip Switched-Capacitor DC-DC Converter Using Digital Capacitance Modulation for LDO Replacement in 45nm CMOS," IEEE ISSSC, 2010
- 2) Michael Seeman et al., "A Comparative Analysis of Switched-Capacitor and Inductor-Based DC-DC Conversion Technologies," Control and Modeling for Power Electronics, 2010


DC-DC Converter Topologies

	Linear (LDO) Regulators	Switched Capacitor Converters	Inductor-based Switching Converters
Fully integrated	✓	✓	✗
High efficiency	✗	✓	✓✓
Voltage Scalability	✓	✗	✓

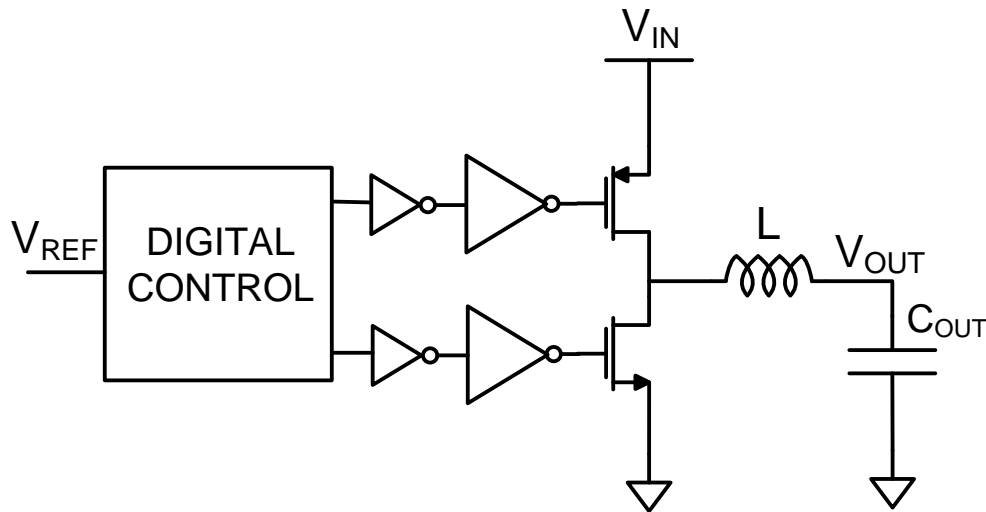

- Needs an external inductor
- Can achieve very high efficiency
- Wide range of output voltages

TPS62736 Buck Converter Architecture

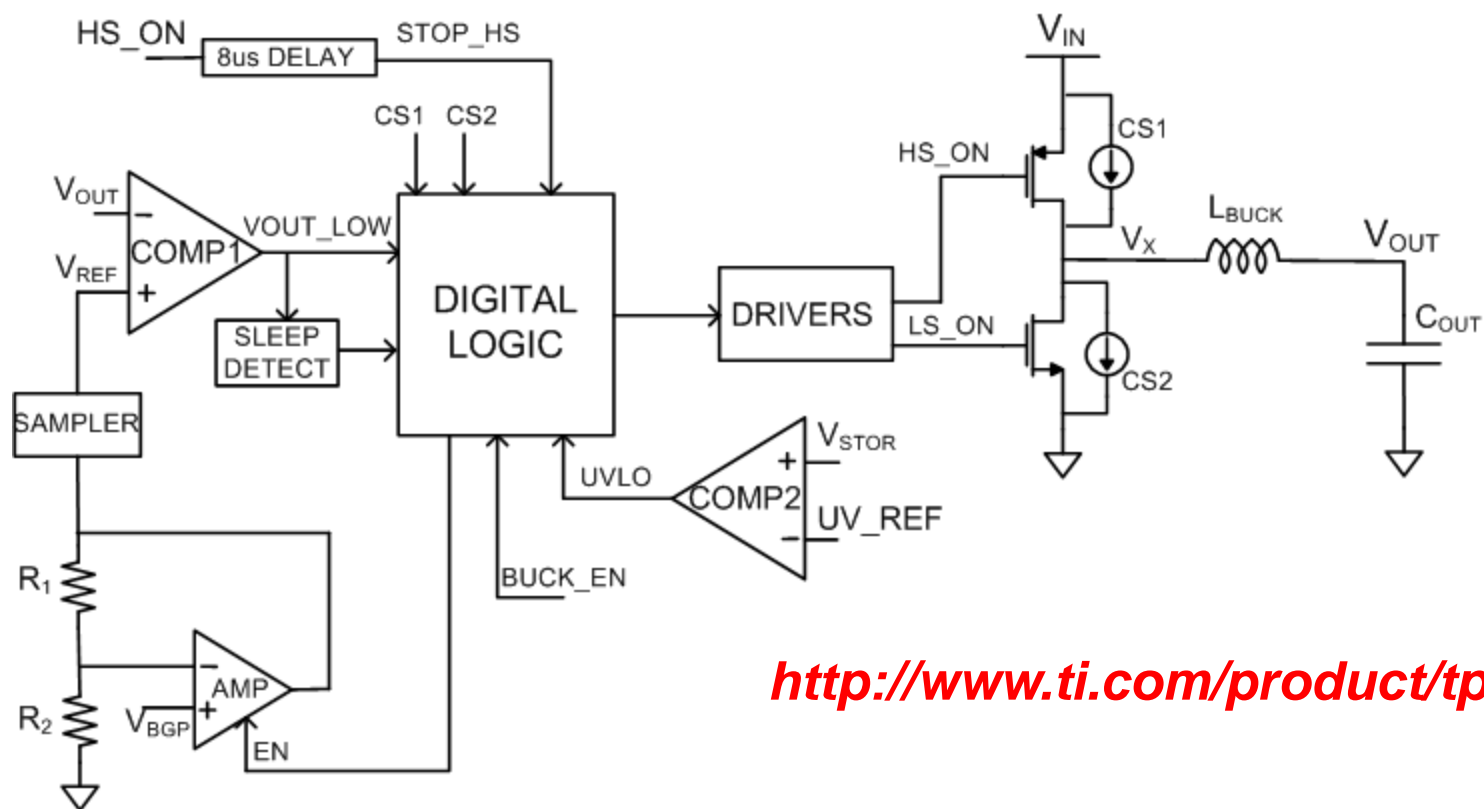


<http://www.ti.com/product/tps62736>

- Main comparator detects if $V_{OUT} < V_{REF}$ to enable converter
- COMP2 detects UV condition to turn off buck
- Sleep detect block to reduce IQ


TPS62736 Buck Converter Efficiency

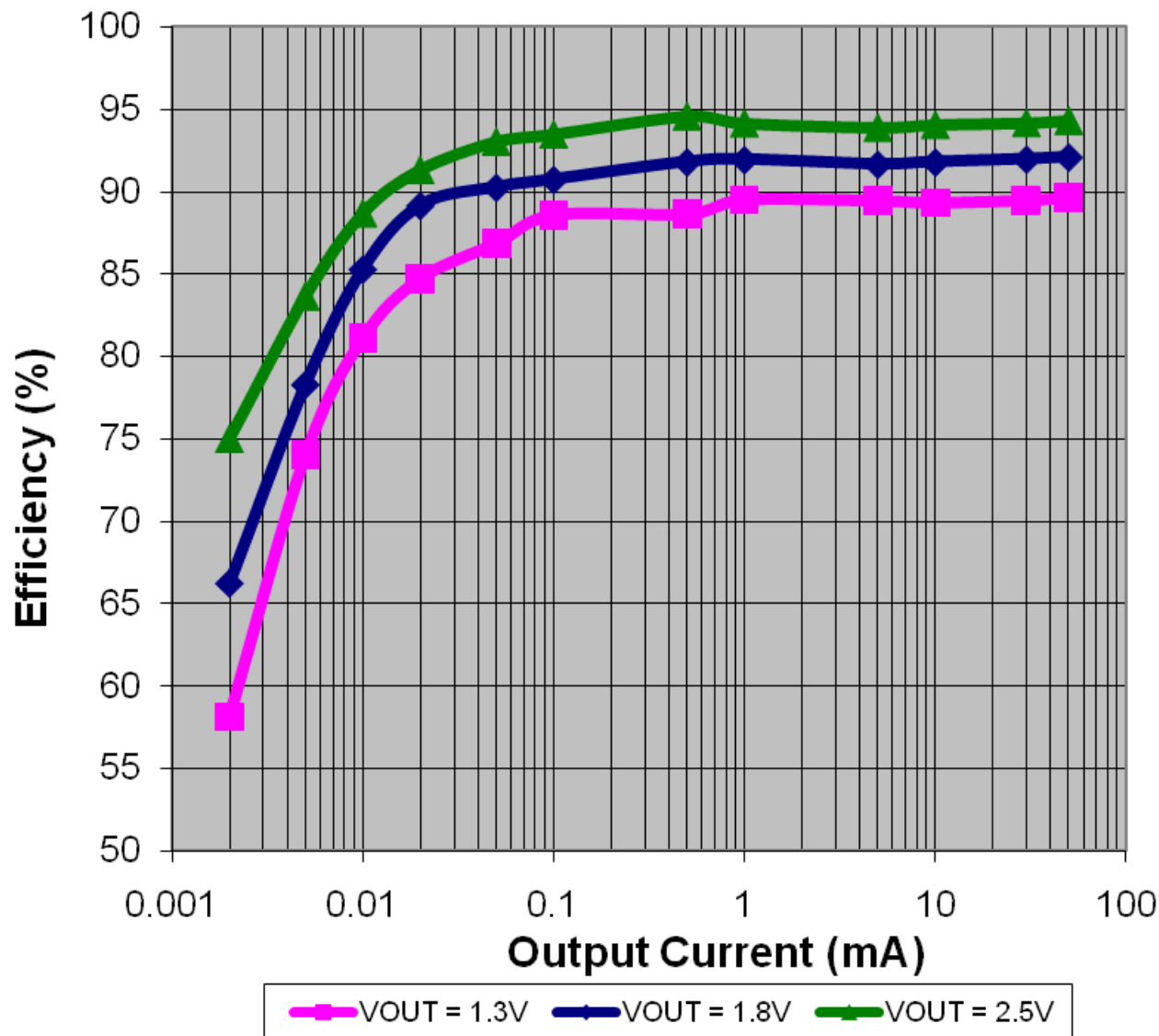Efficiency vs. Output Current ($V_{IN} = 3V$)




- Maintains constant efficiency from 20 μA to 50mA
- >80% down to 10 μA
- $I_Q = 360nA$

Battery Management and Peripherals

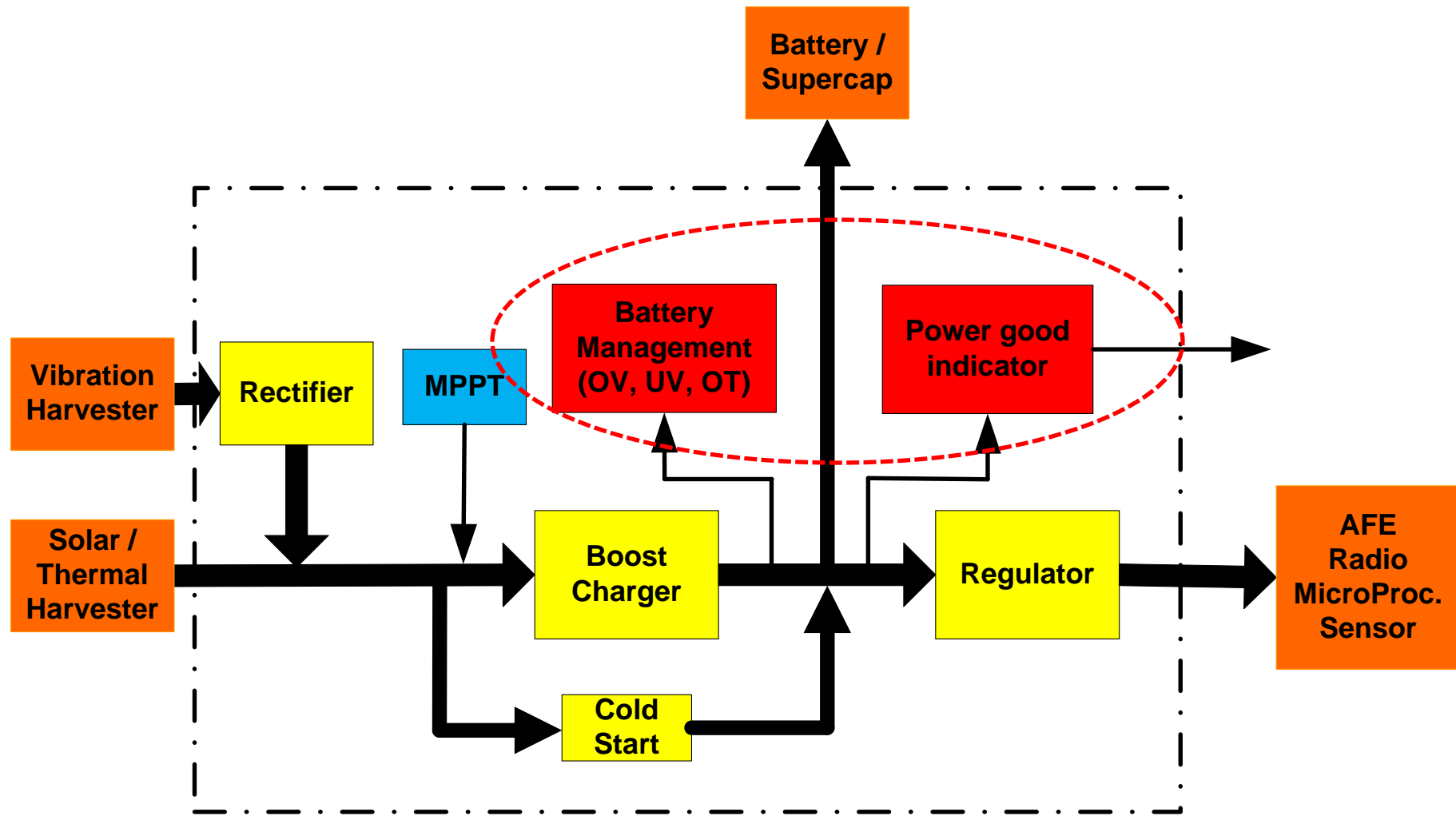


Protect the storage element, manage the IC and indicate level of stored energy

BQ25570 Essential Peripheral Circuits

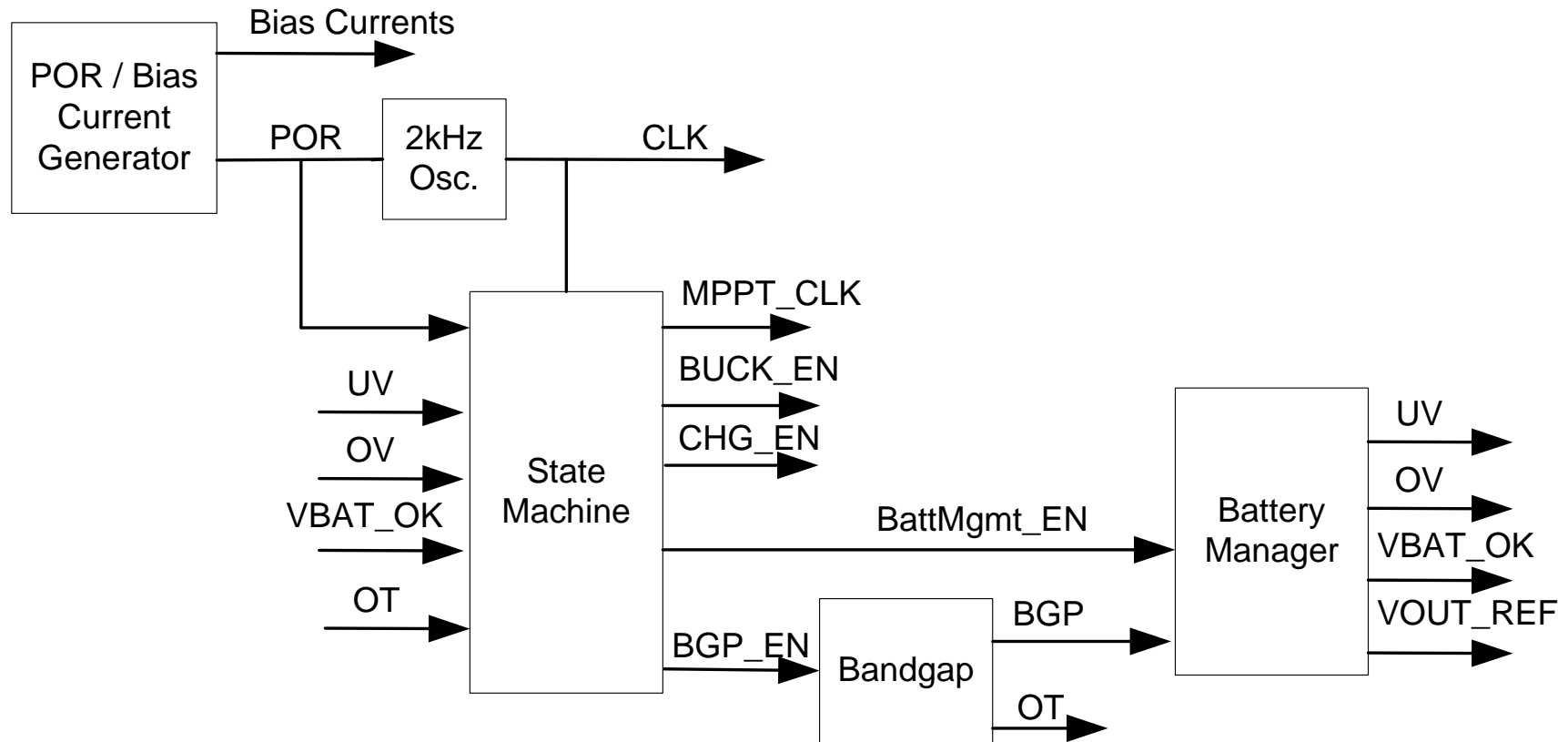


- All circuits run off VSTOR
- Perform essential startup and general maintenance of IC

Main Oscillator

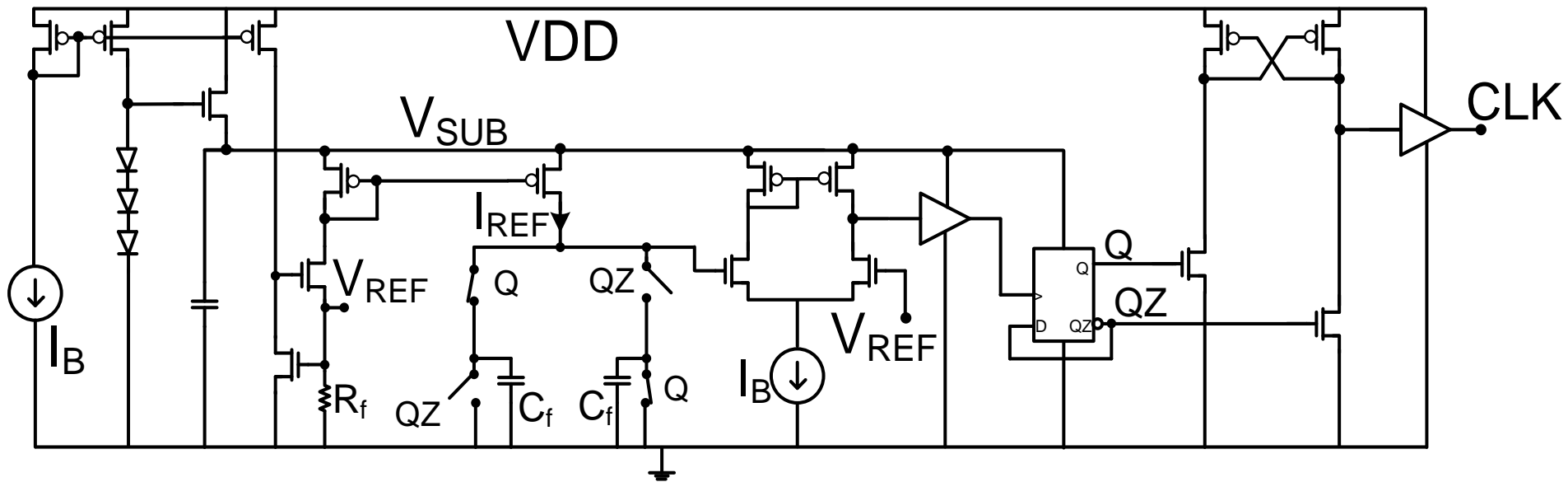


- Relaxation oscillator frequency $\sim 2\text{kHz}$
- Sub-regulation reduces quiescent current
- **$I_Q = 50\text{nA}$ @ 27°C and 100nA across temperature**

Battery Mgmt. Architecture

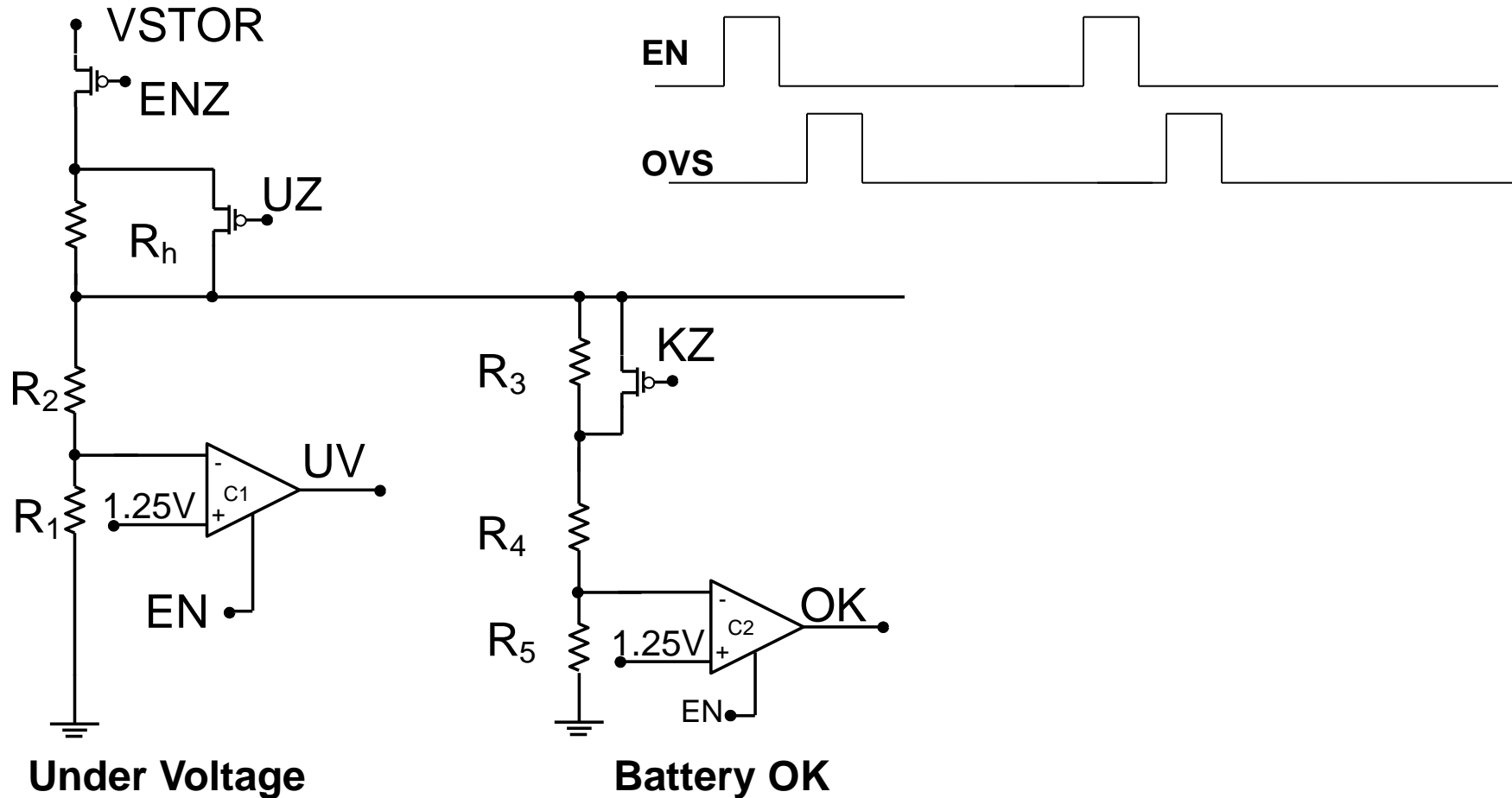


- Resistor programmable **UV**, **OK**, **OV**
- Cycle repeats every 64ms
- Duty cycled and sampled reference

Battery Mgmt. Architecture

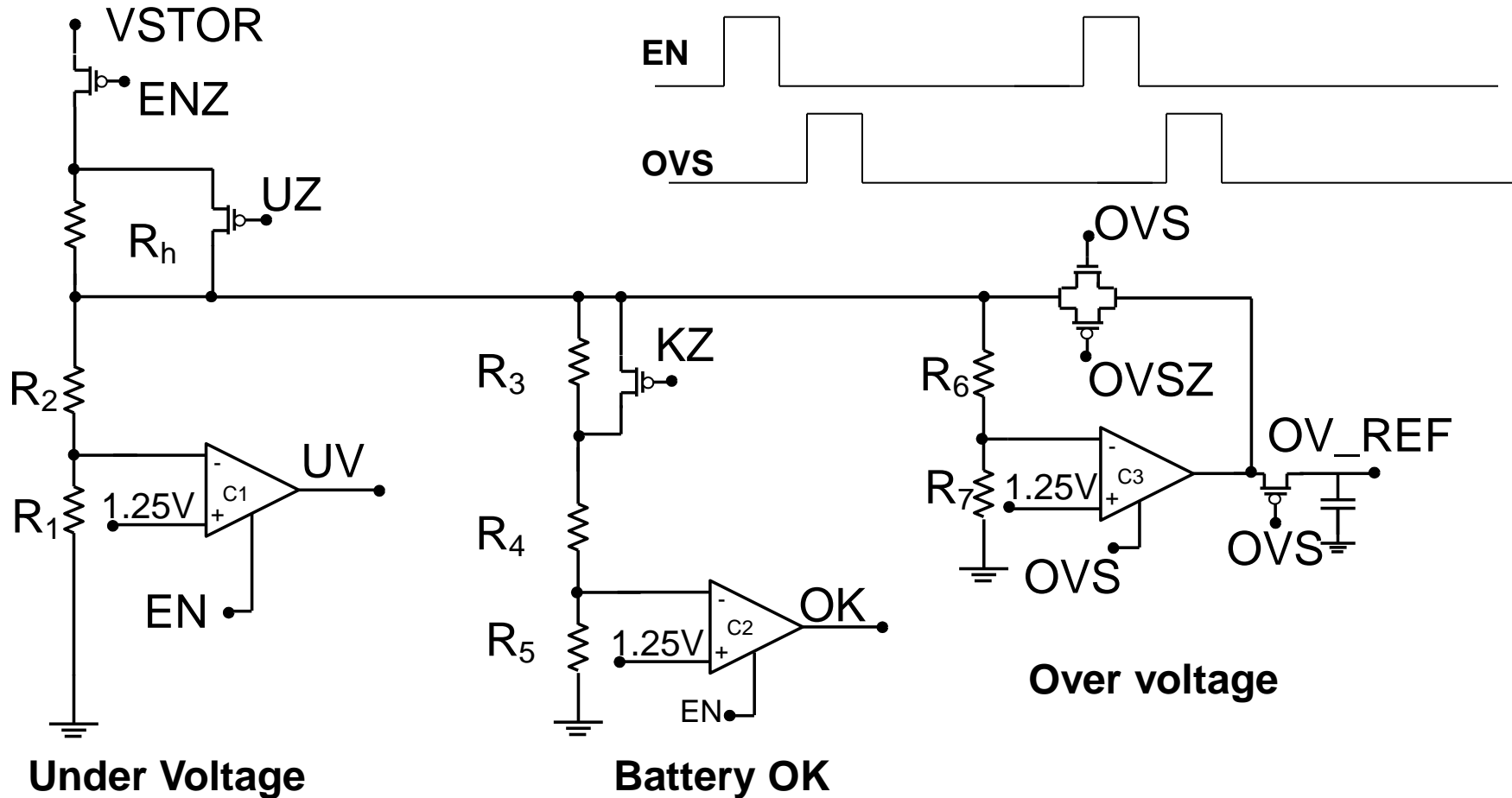

- Resistor programmable **UV**, **OK**, **OV**
- Cycle repeats every 64ms
- Duty cycled and sampled reference


BQ25570 Quiescent Current

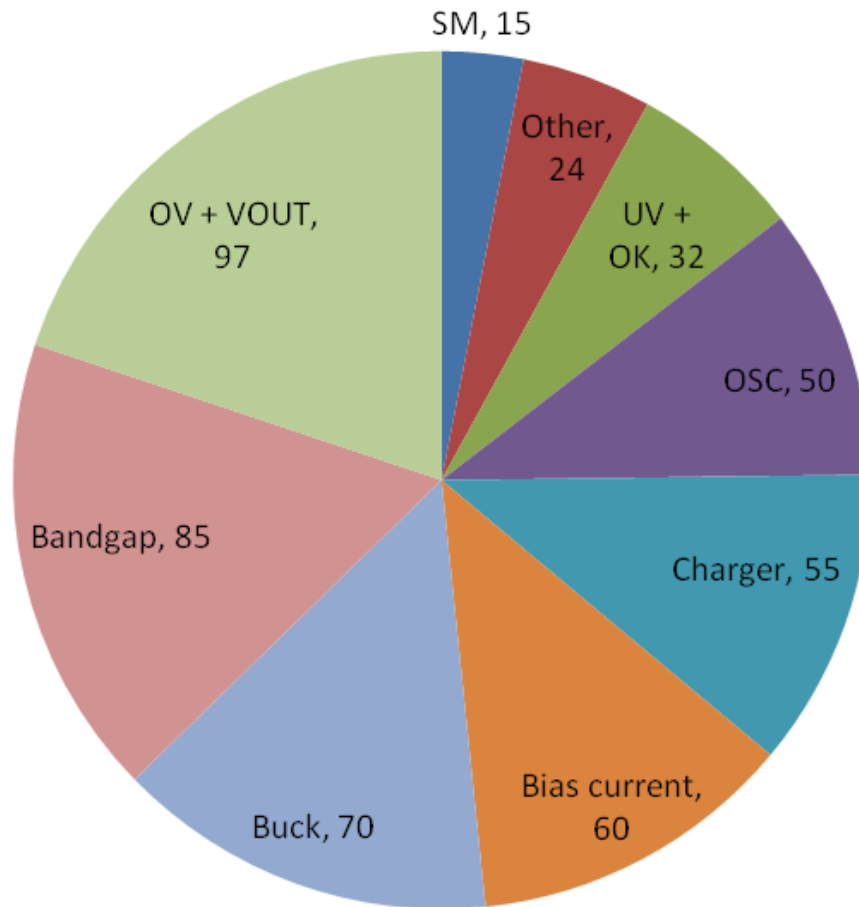


- VBAT = 3V
- Overall Quiescent current : **480nA**
- Battery leakage below UV = **1nA**

Currents in nA

BQ25570 System Startup

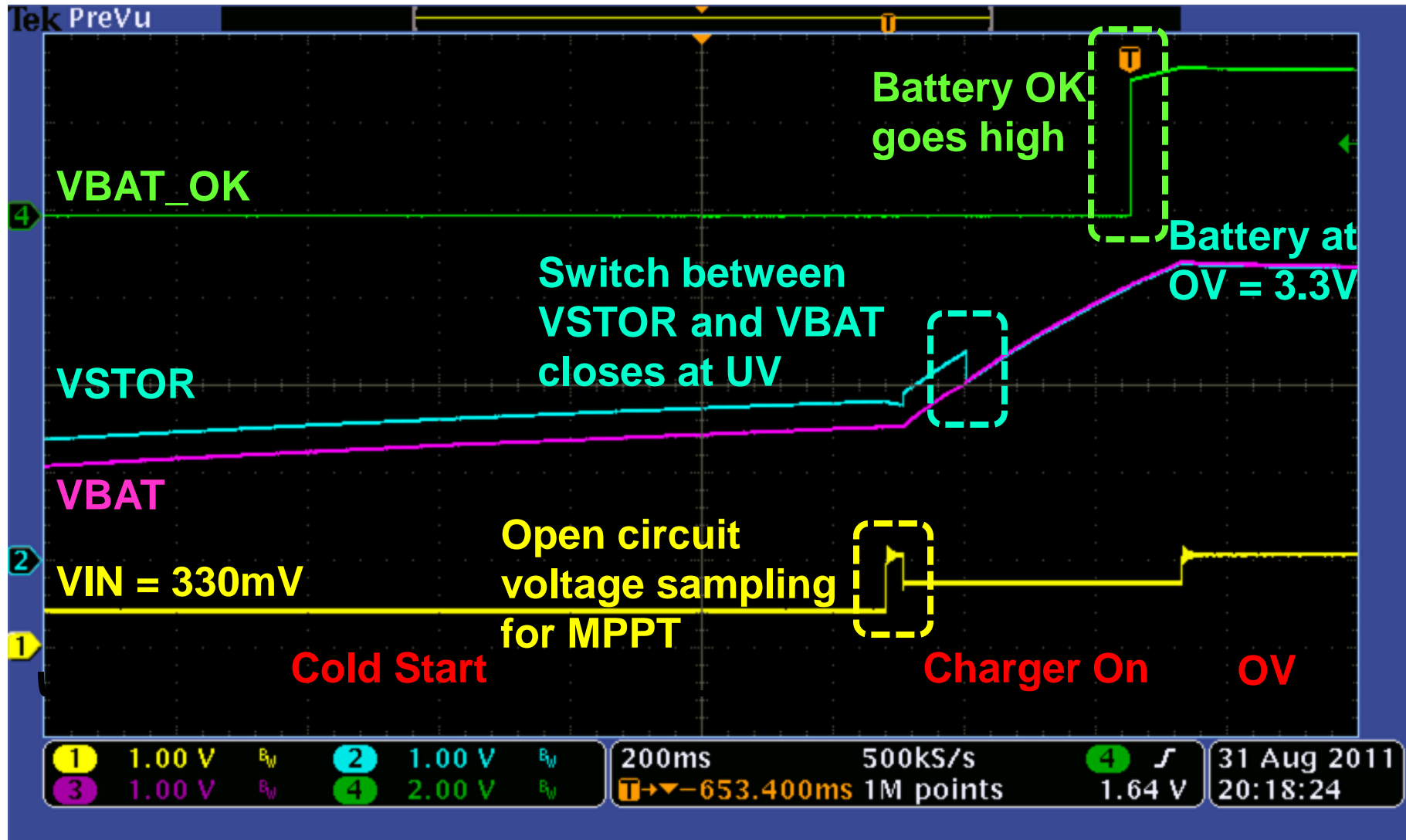

Energy Harvesting with Battery Backup

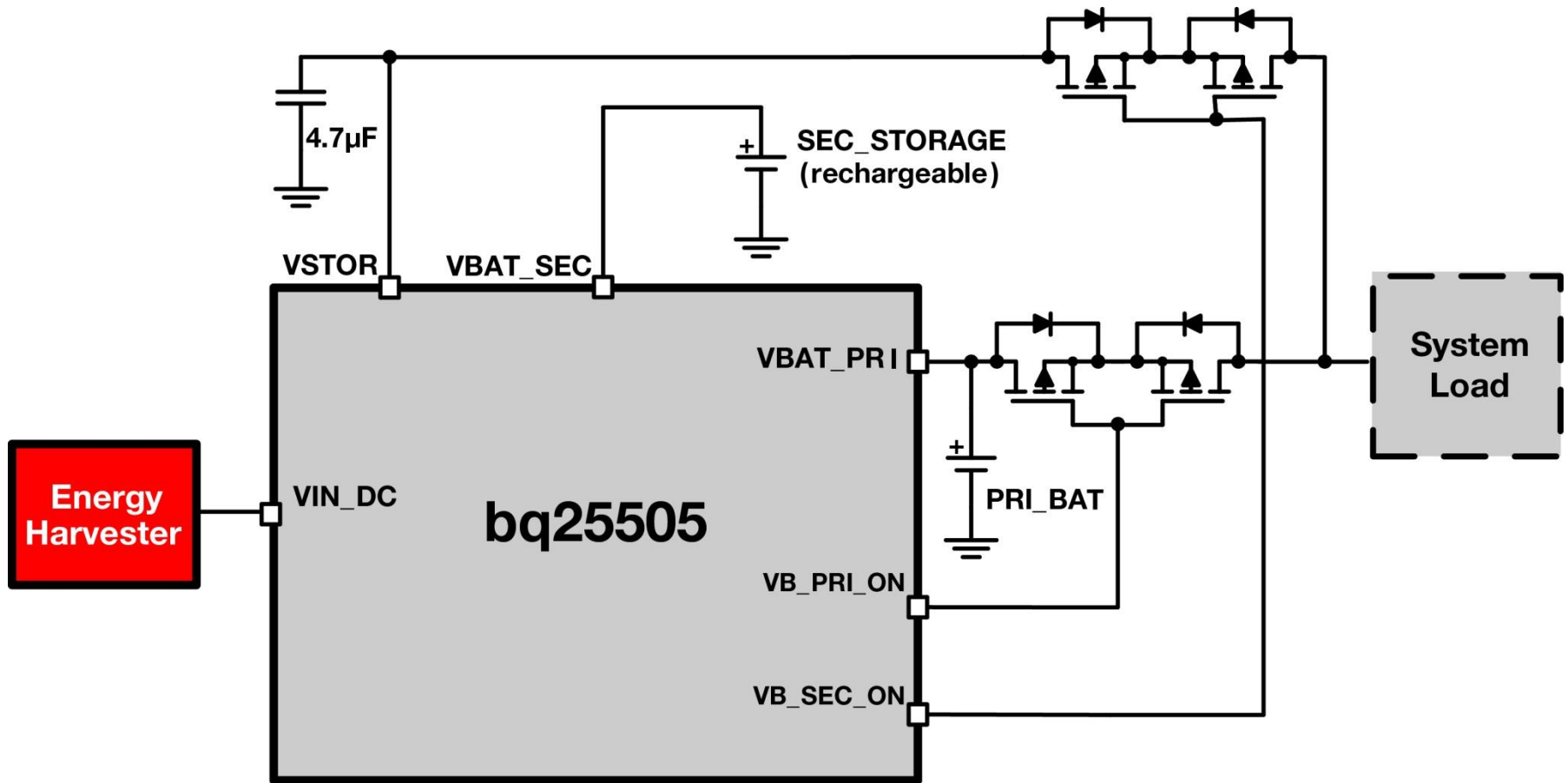


<http://www.ti.com/product/bq25505>


Autonomous handoff between primary and secondary storage

Dual-Path Energy Harvesting

Conventional

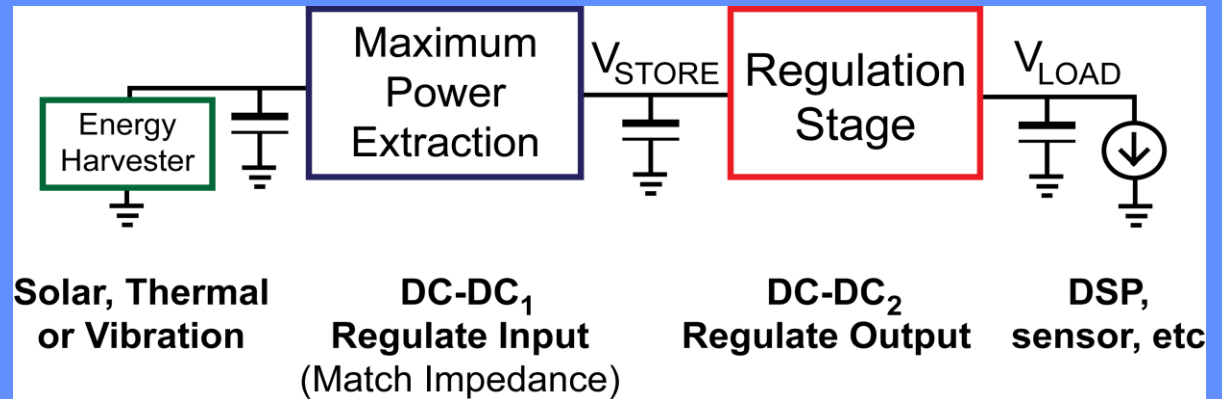



DP

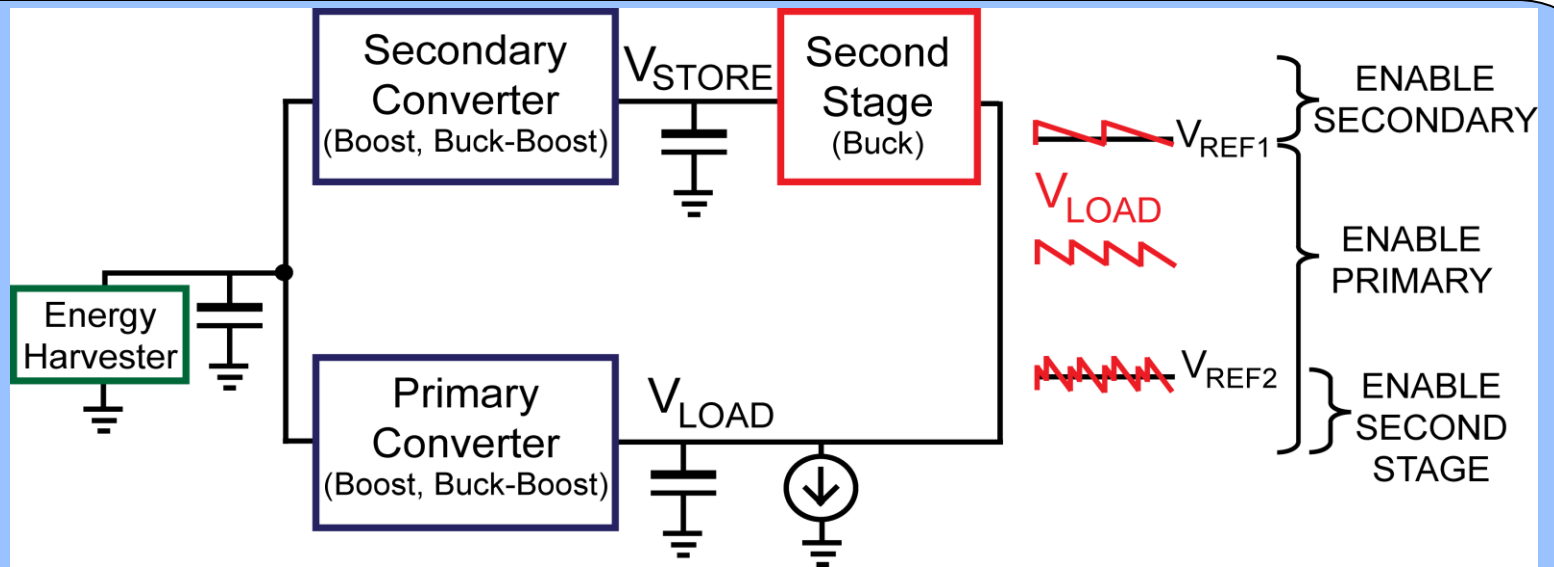

Bypassing Second Stage results in 13% peak efficiency improvement


[S.Bandyopadhyay, VLSI Symposium 2011]

Inductor Sharing

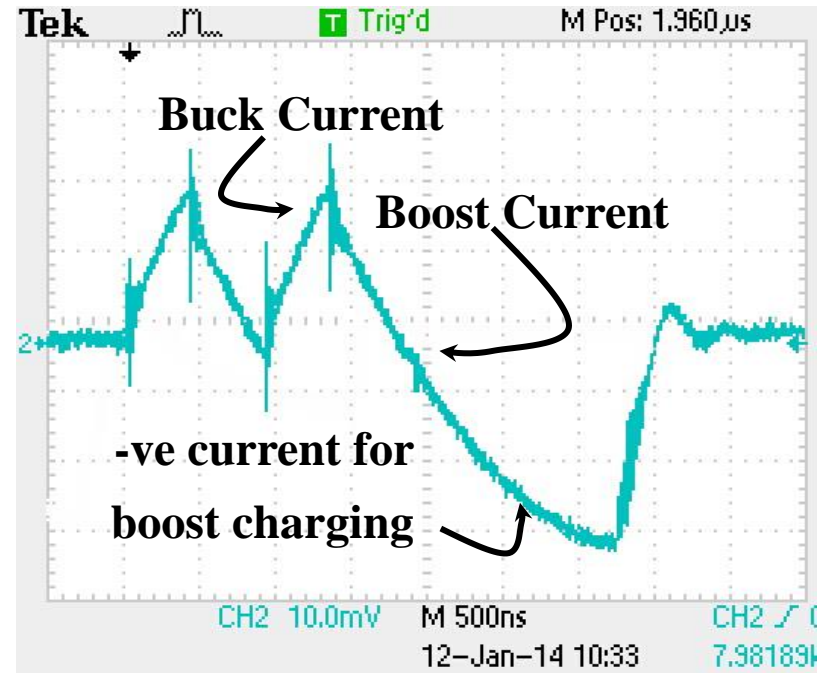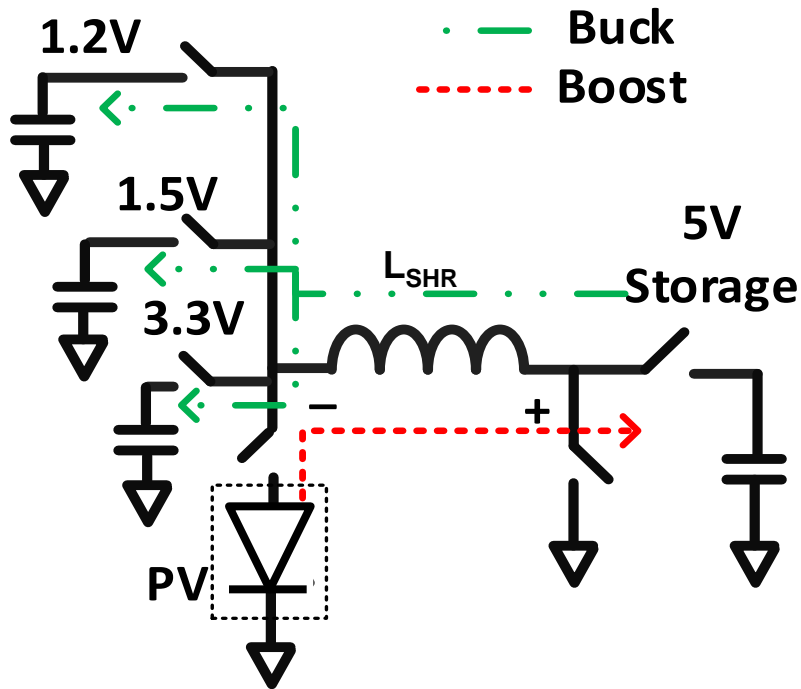

- A single inductor is used for boost conversion as well as for generating multiple regulated output voltages

Energy Combining

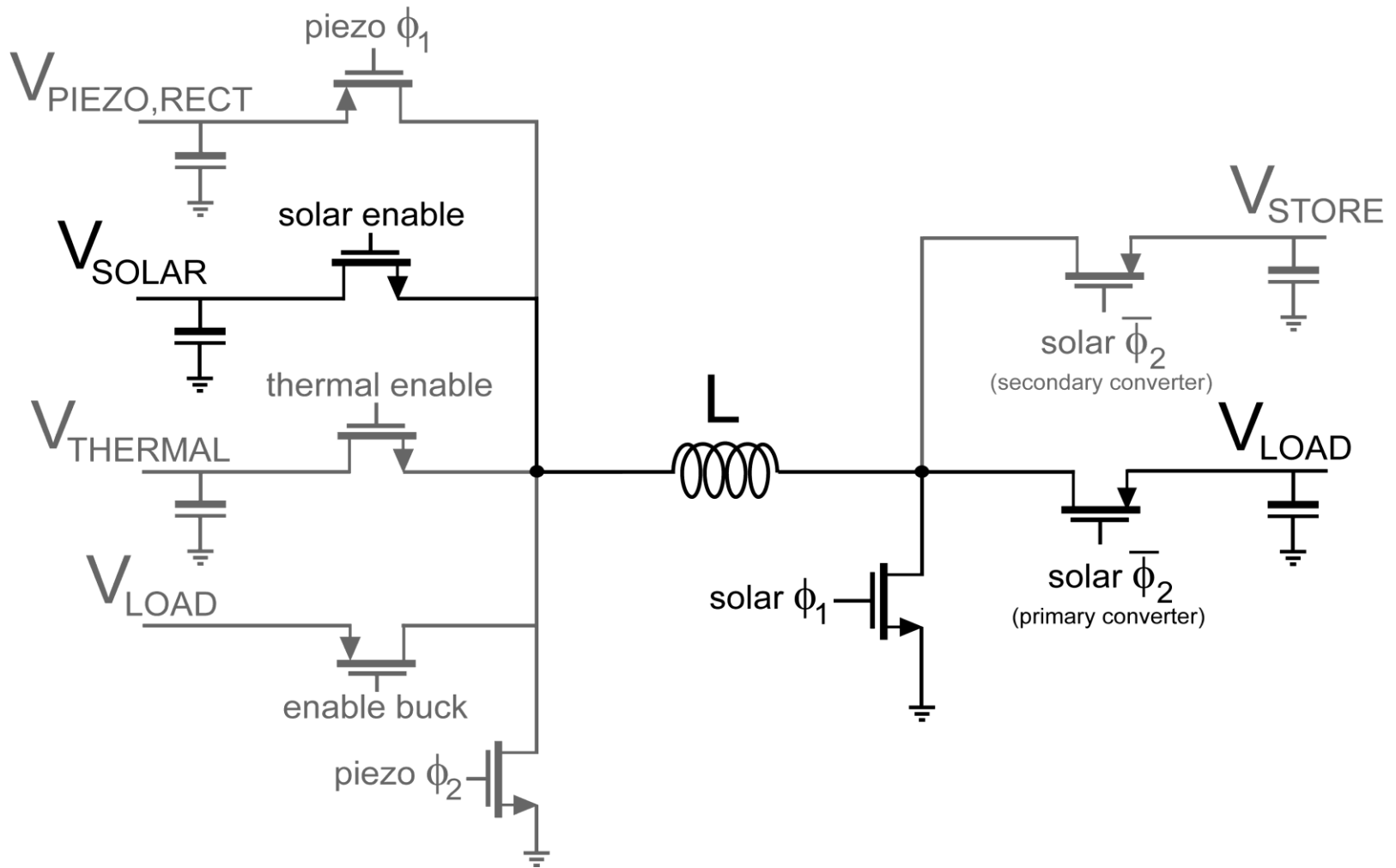

Shared inductor minimizes board components

Summary

- Advances in circuit design techniques and architectures have made it possible for electronic systems to be completely self-powered
- Energy harvesting sources differ in characteristics from conventional batteries requiring specialized interface circuits
- Optimized energy processing circuits are crucial to manage the ultra-low power levels output by energy harvesters
- Holistic optimization of the complete system from the energy sources to the load circuits is key to building a successful IoT system